


# Parallel *LR* Circuits

*Carl E. Mungan, Physics Dept, U.S. Naval Academy, Annapolis MD*

Fall Meeting of the Chesapeake Section  
of the American Association of Physics Teachers

Saturday 11 October 2025 at Virginia Commonwealth University


## First circuit

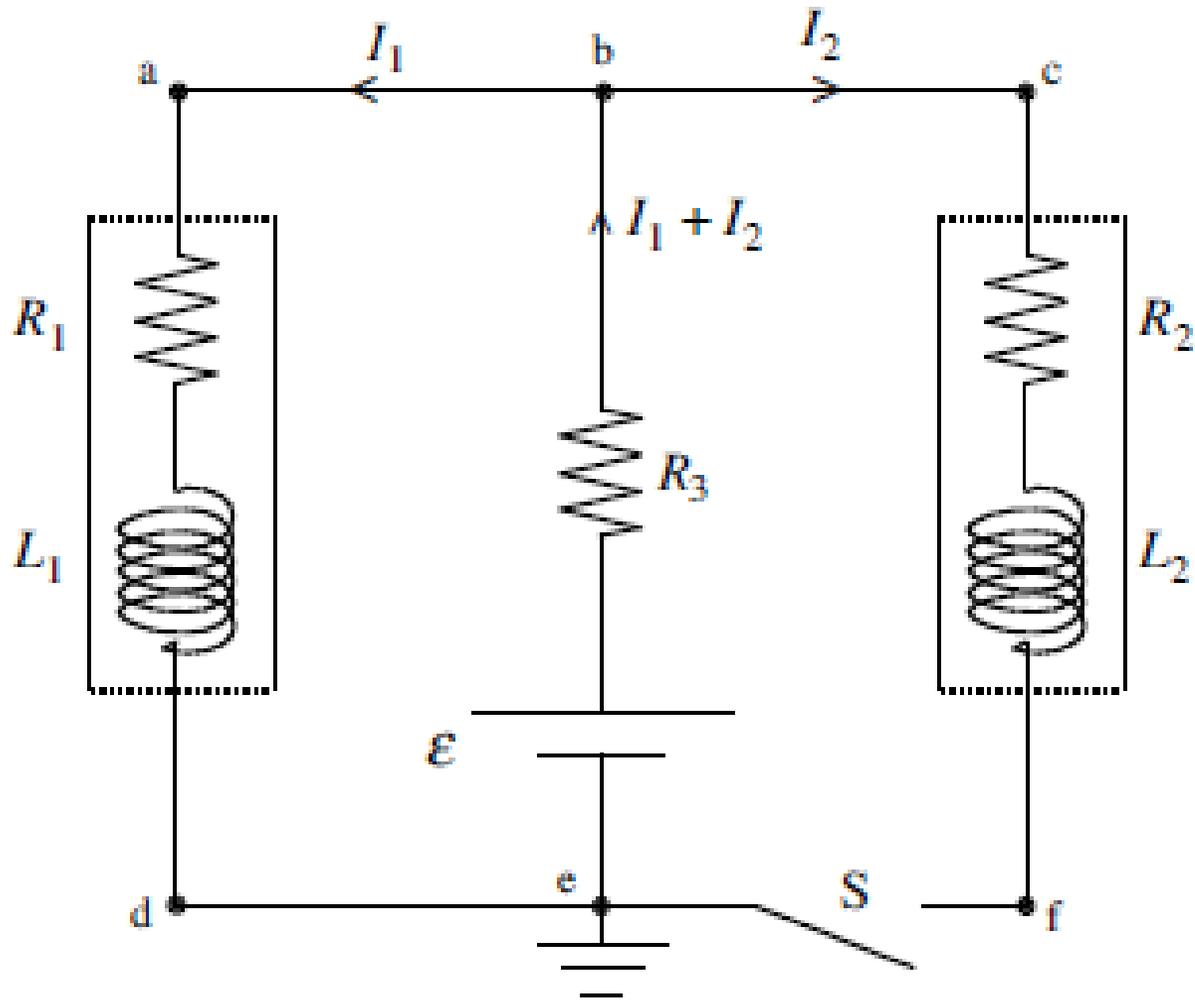

Two coils (indicated by the rectangles) each have inductance and resistance.

What happens if  $R_3 = 0$ ?

## First circuit

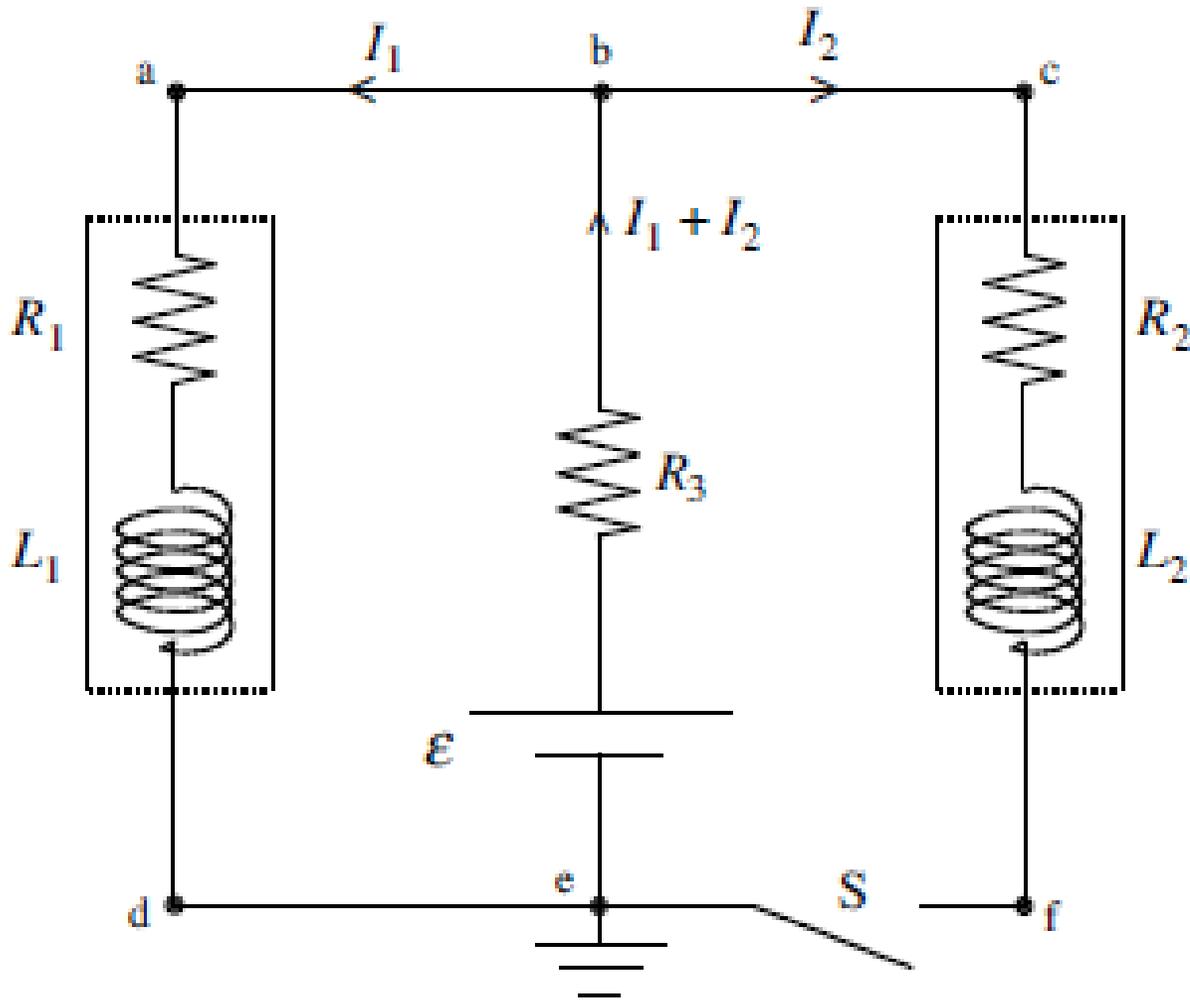

Two coils (indicated by the rectangles) each have inductance and resistance.


What happens if  $R_3 = 0$ ?

Then the two coils *independently* have the battery connected (or not) across them.

Resistor  $R_3$  *couples* together the two currents through the coils.


Consider the current through coil 1, starting from when we close S after it has been open for a long time:
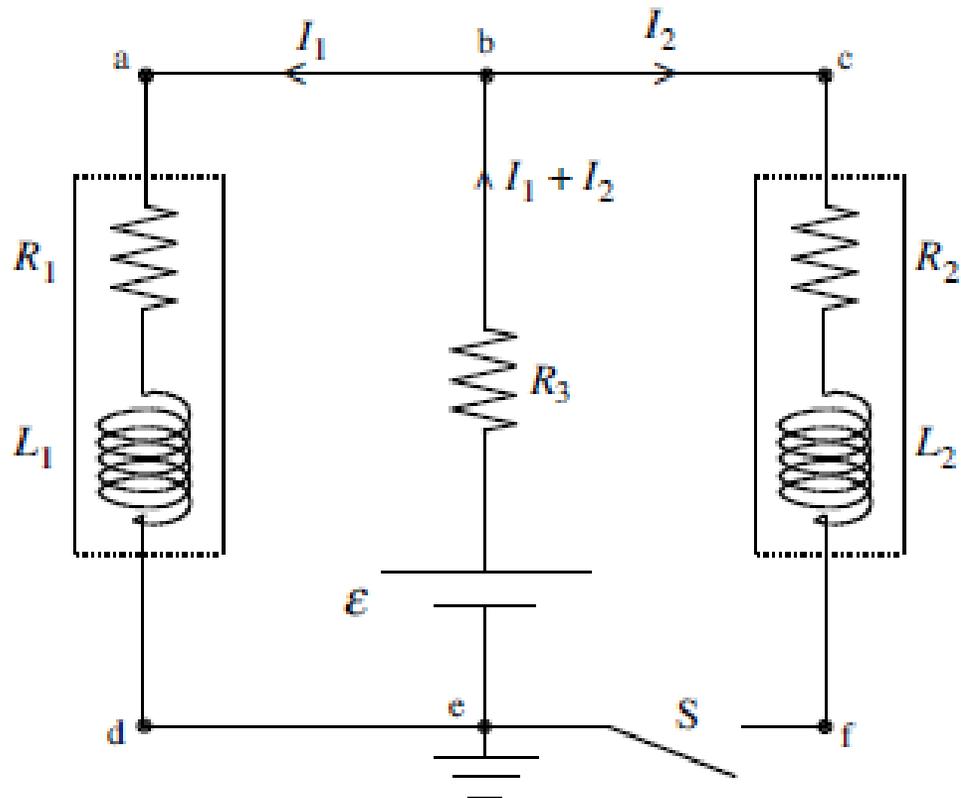
$$I_1(0) = \frac{\varepsilon}{R_1 + R_2} \quad \frac{dI_1}{dt}(0) = 0 \quad I_1(\infty) = \frac{\varepsilon R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$



Consider the current through coil 1, starting from when we close S after it has been open for a long time:
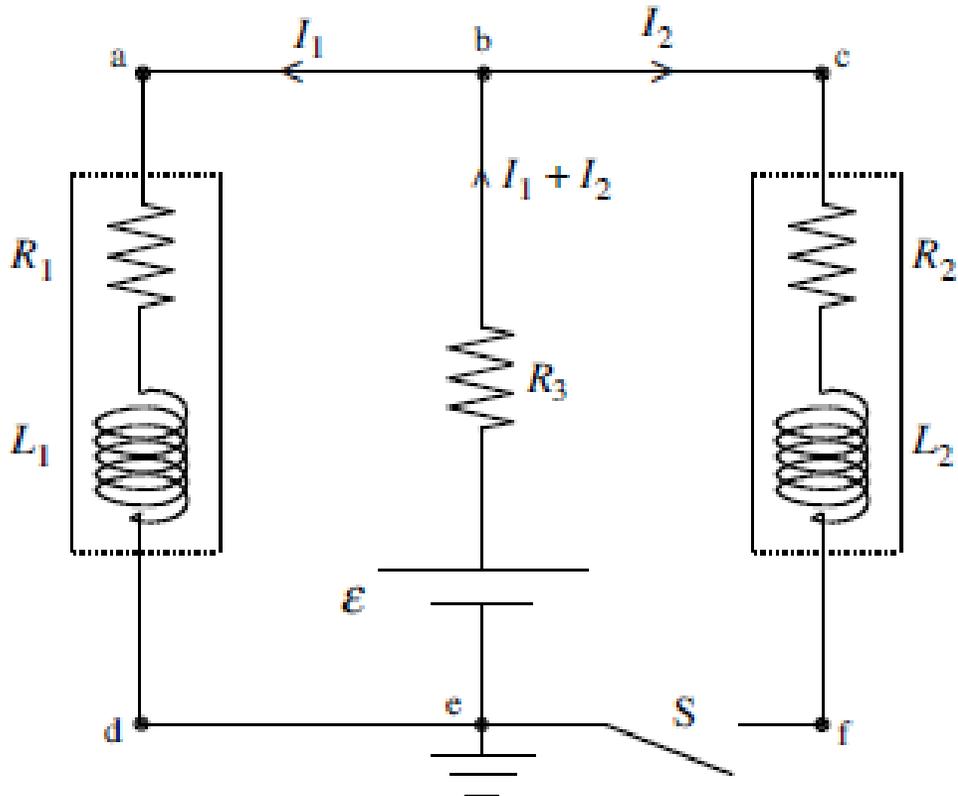
$$I_1(0) = \frac{\varepsilon}{R_1 + R_2} \quad \frac{dI_1}{dt}(0) = 0 \quad I_1(\infty) = \frac{\varepsilon R_2}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$



Write down KVL for the left and right loops. Eliminate  $I_2$  between them to get a second order DE for  $I_1$  whose solution is a double exponential:

$$I_1(t) = C_{\text{slow}} \exp(-k_{\text{slow}}t) + C_{\text{fast}} \exp(-k_{\text{fast}}t) + I_1(\infty)$$

where  $C_{\text{slow}}$  is positive,  $C_{\text{fast}}$  is negative, and  $|C_{\text{slow}}| > |C_{\text{fast}}|$ .

experimental values:

$$L_1 = L_2 = 4.0 \text{ H}$$


$$R_1 = R_2 = 89 \ \Omega$$

$$R_3 = 200 \ \Omega$$

$$\varepsilon = 9.3 \text{ V}$$

With coil 1 in place, we get a double exponential with zero initial slope.

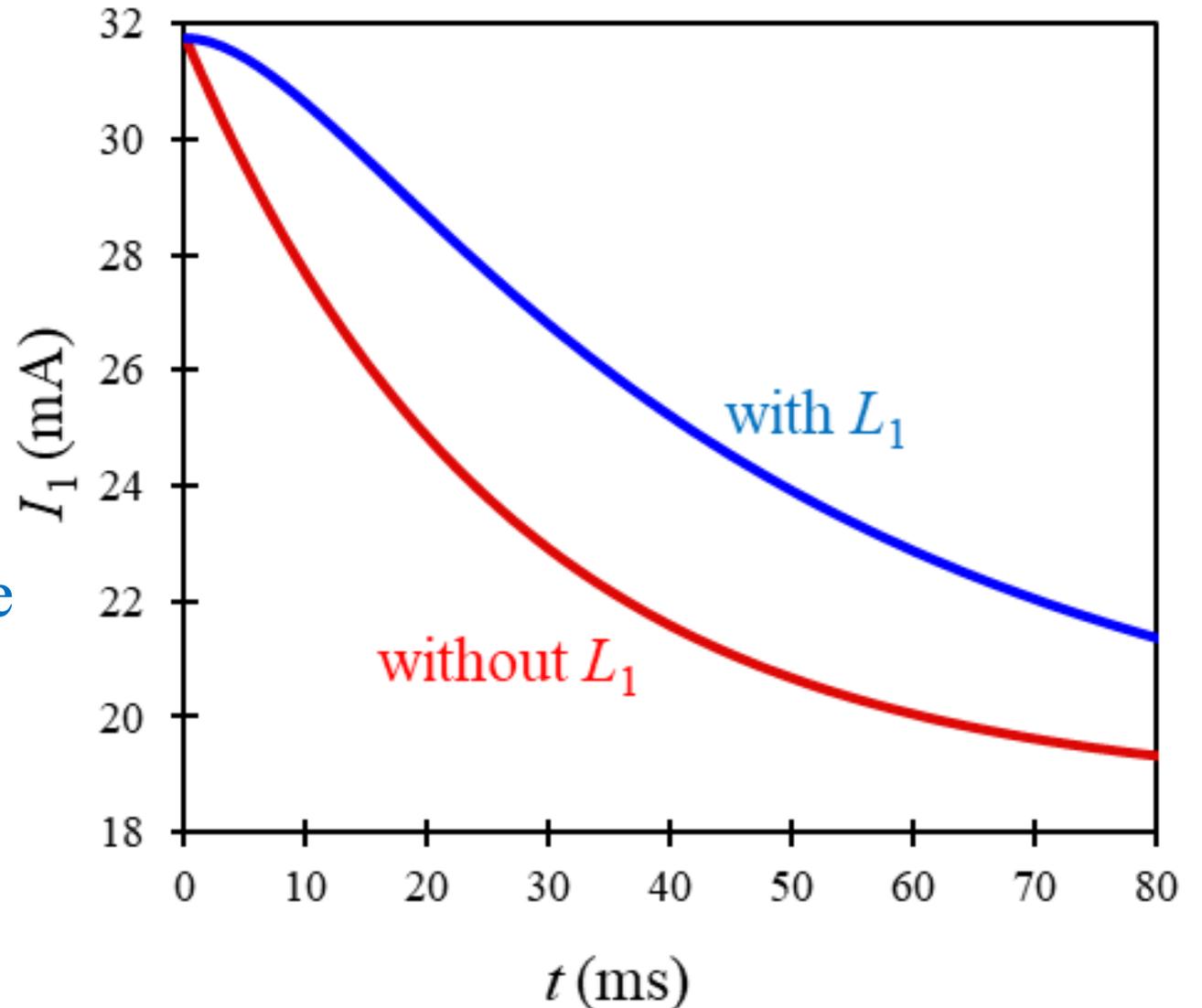Replace coil 1 with an  $89 \ \Omega$  resistor to get a single exponential.




For such a case of identical coils with  $L_1 = L_2 = L$  and  $R_1 = R_2 = R$  we get symmetric and antisymmetric modes:

$$I_1 + I_2 \propto \exp(-k_{\text{fast}} t) \quad \text{and} \quad I_1 - I_2 \propto \exp(-k_{\text{slow}} t)$$

$$\text{where } k_{\text{fast}} = \frac{R_{\text{equiv}}}{L_{\text{equiv}}} = \frac{R/2 + R_3}{L/2} \quad \text{and} \quad k_{\text{slow}} = \frac{R}{L}$$

(see *Physics Challenges for Teachers and Students*  
in May 2004 issue of the *Physics Teacher*)

## Second circuit

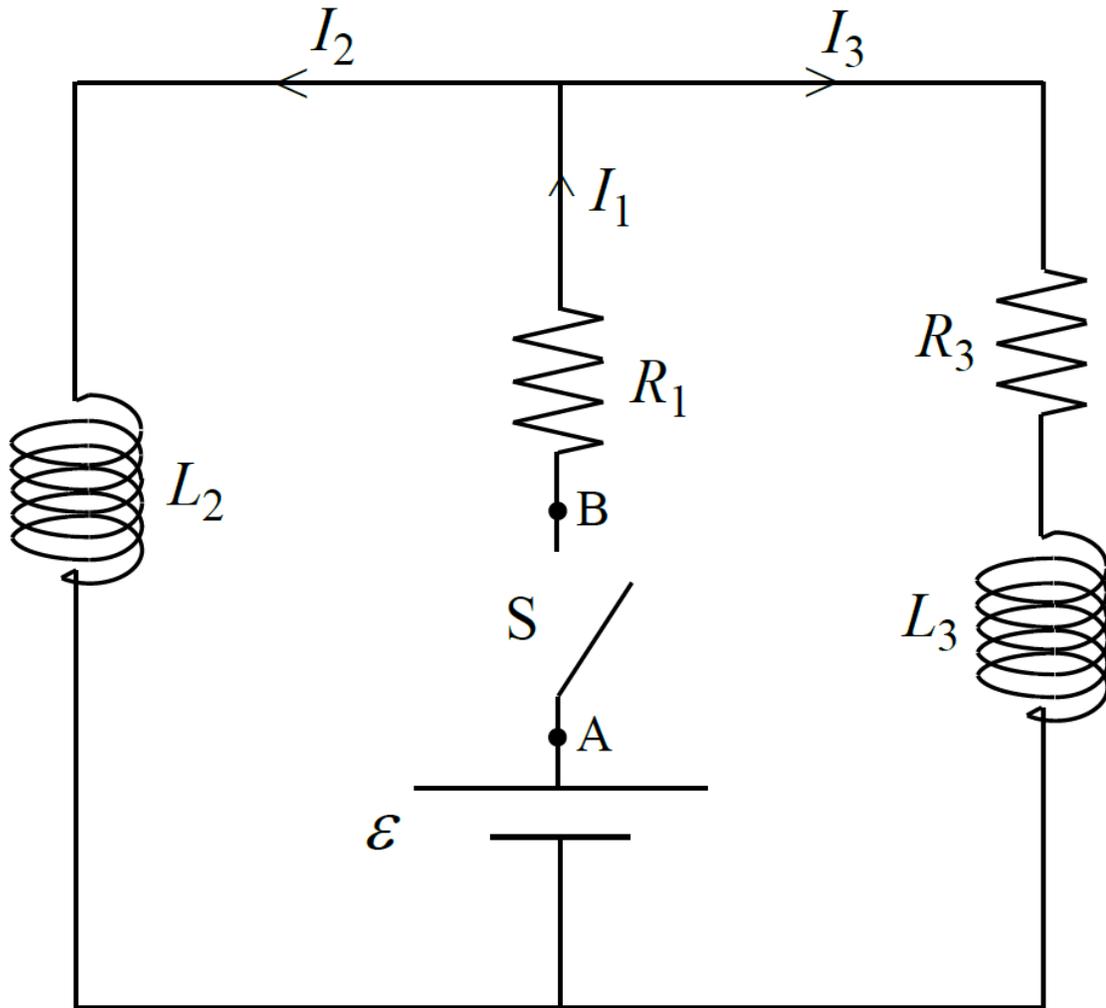

compared to first circuit:


- switch moved into center branch
- resistance of left coil is negligible

switch  $S$  open for a long time:

$$I_1(0) = 0, \quad I_2(0) = 0, \quad I_3(0) = 0$$

What will the currents be if  $S$  is closed for a long time?

## Second circuit

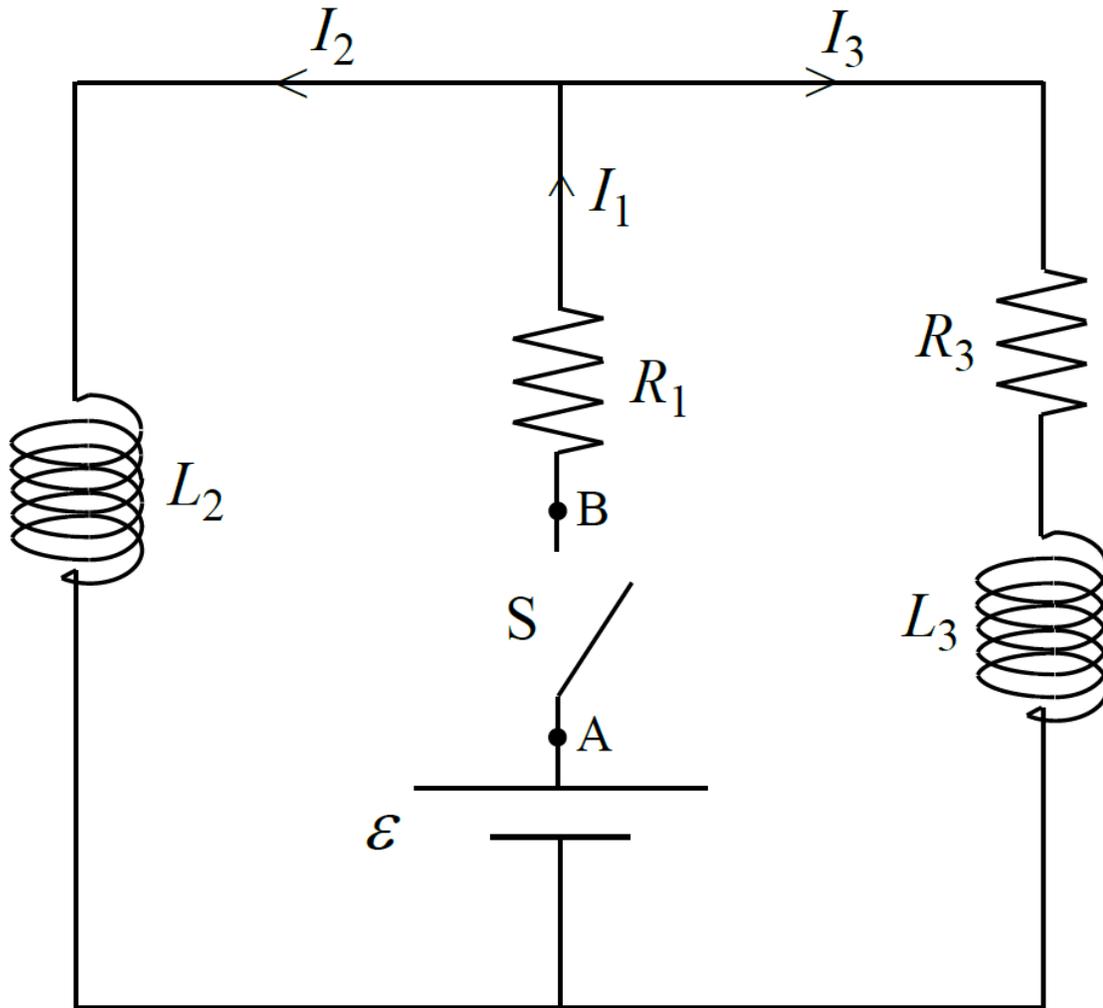

- compared to first circuit:
- switch moved into center branch
  - resistance of left coil is negligible

switch S open for a long time:

$$I_1(0) = 0, \quad I_2(0) = 0, \quad I_3(0) = 0$$

What will the currents be if S is closed for a long time?

$I_2$  becomes constant  $\Rightarrow$

voltage across  $L_2$  becomes zero

$$\therefore I_3(\infty) = 0 \Rightarrow$$


$$I_1(\infty) = I_2(\infty) = \varepsilon / R_1$$

Analyze circuit starting from the instant S is closed  
using Kirchhoff's laws to get:


$$R_1 = R_3 = 1 \Omega$$

$$L_2 = L_3 = 1 \text{ H}$$

$$\varepsilon = 1 \text{ V}$$

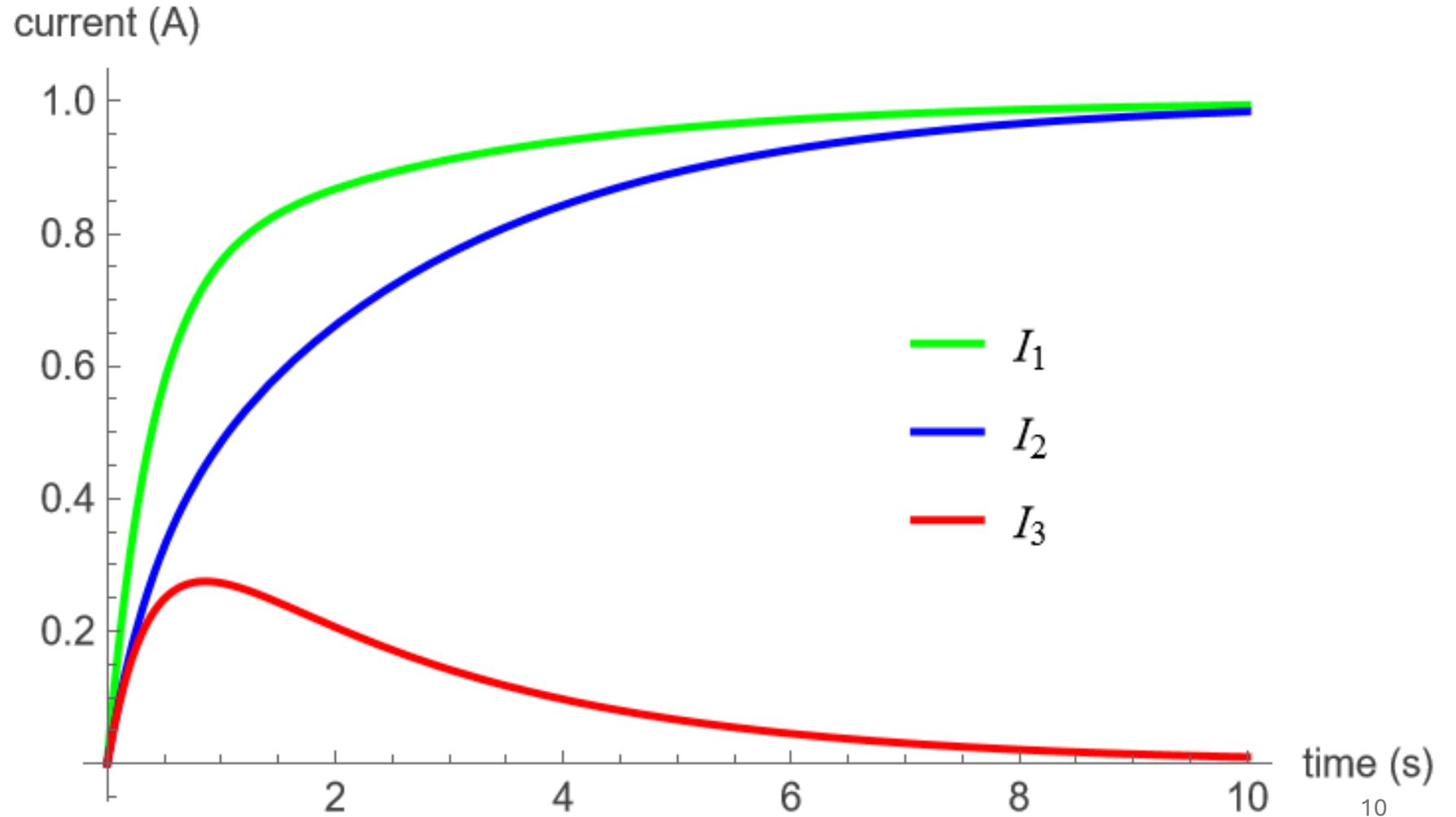


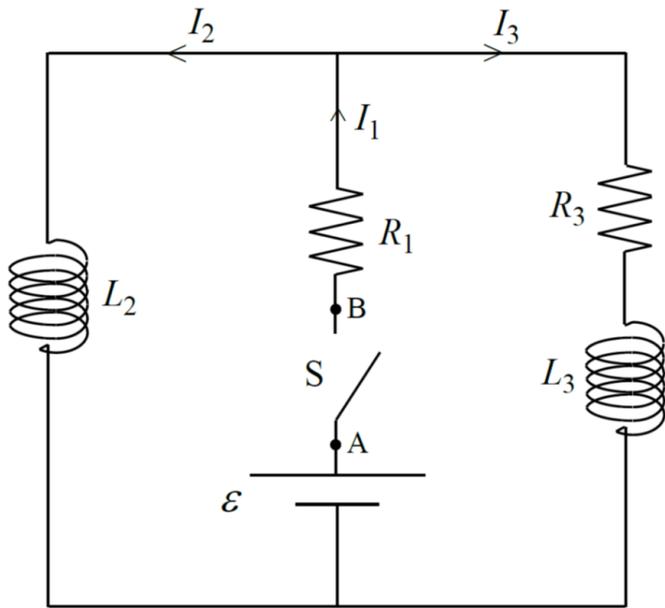After S has been closed for a long time, open it.  
Now what are the three time-dependent currents?



After S has been closed for a long time, open it.  
Now what are the three time-dependent currents?

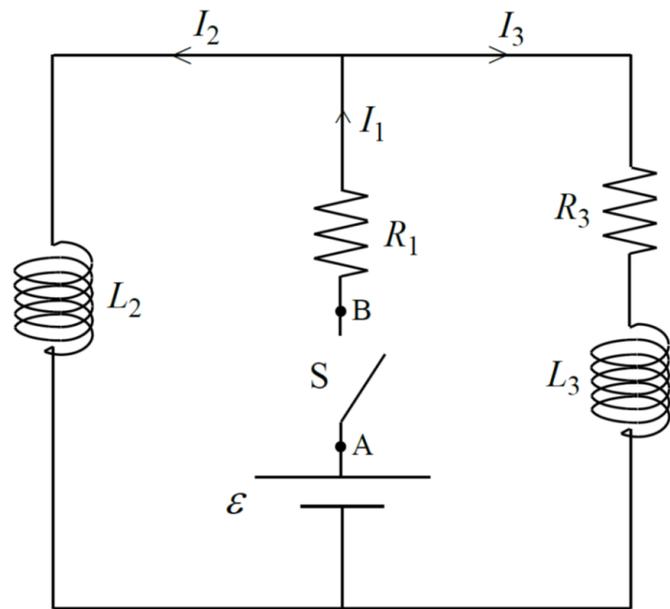redefine  $t = \infty$  as  $t = 0$  so  $I_2(0) = \varepsilon / R_1$  and  $I_3(0) = 0$  maintained thru the inductors




but S interrupts the middle current so  $I_1(0) = 0$

contradiction! those currents violate  $I_1 = I_2 + I_3$

After S has been closed for a long time, open it.  
Now what are the three time-dependent currents?

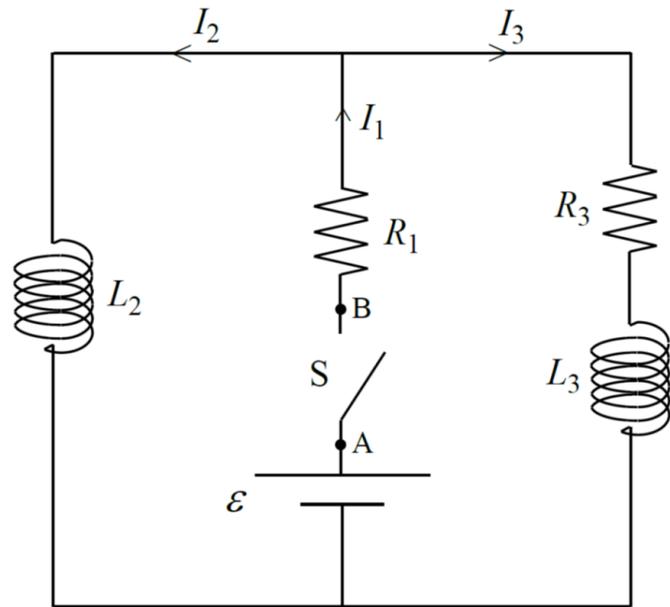redefine  $t = \infty$  as  $t = 0$  so  $I_2(0) = \varepsilon / R_1$  and  $I_3(0) = 0$  maintained thru the inductors




but S interrupts the middle current so  $I_1(0) = 0$

contradiction! those currents violate  $I_1 = I_2 + I_3$

If you tried this with a real circuit,  
a spark would arc across S to try to maintain  $I_1$ .  
So the fix is to replace S with a switch that  
turns off  $I_1$  gradually instead of instantly.

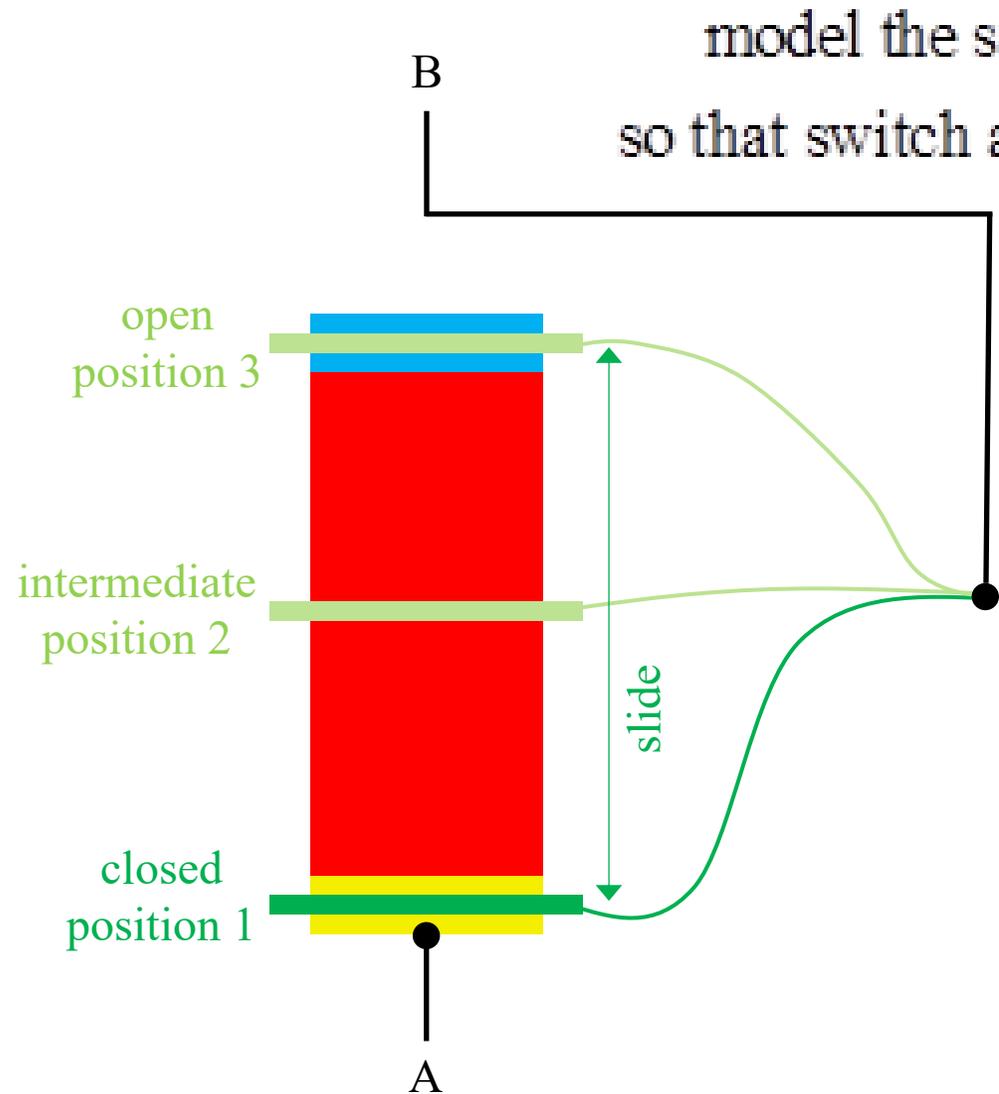Modified switch: zero resistance in position 1 and infinite resistance in position 3.



model the slide as a linear increase at rate constant  $k$   
so that switch and resistor together has resistance  $(1 + kt)R_1$

$\therefore$  resistance is  $R_1$  at  $t = 0$   
and infinite at  $t = \infty$   
(as desired)

Reanalyze circuit numerically starting from the instant S is opened using Kirchhoff's laws to get:

$$R_1 = 1 \Omega$$


$$R_3 = 1 \text{ k}\Omega$$

$$L_2 = 1 \text{ H}$$

$$L_3 = 1 \text{ mH}$$

$$\varepsilon = 1 \text{ V}$$

$$k = 10^9 \text{ s}^{-1}$$

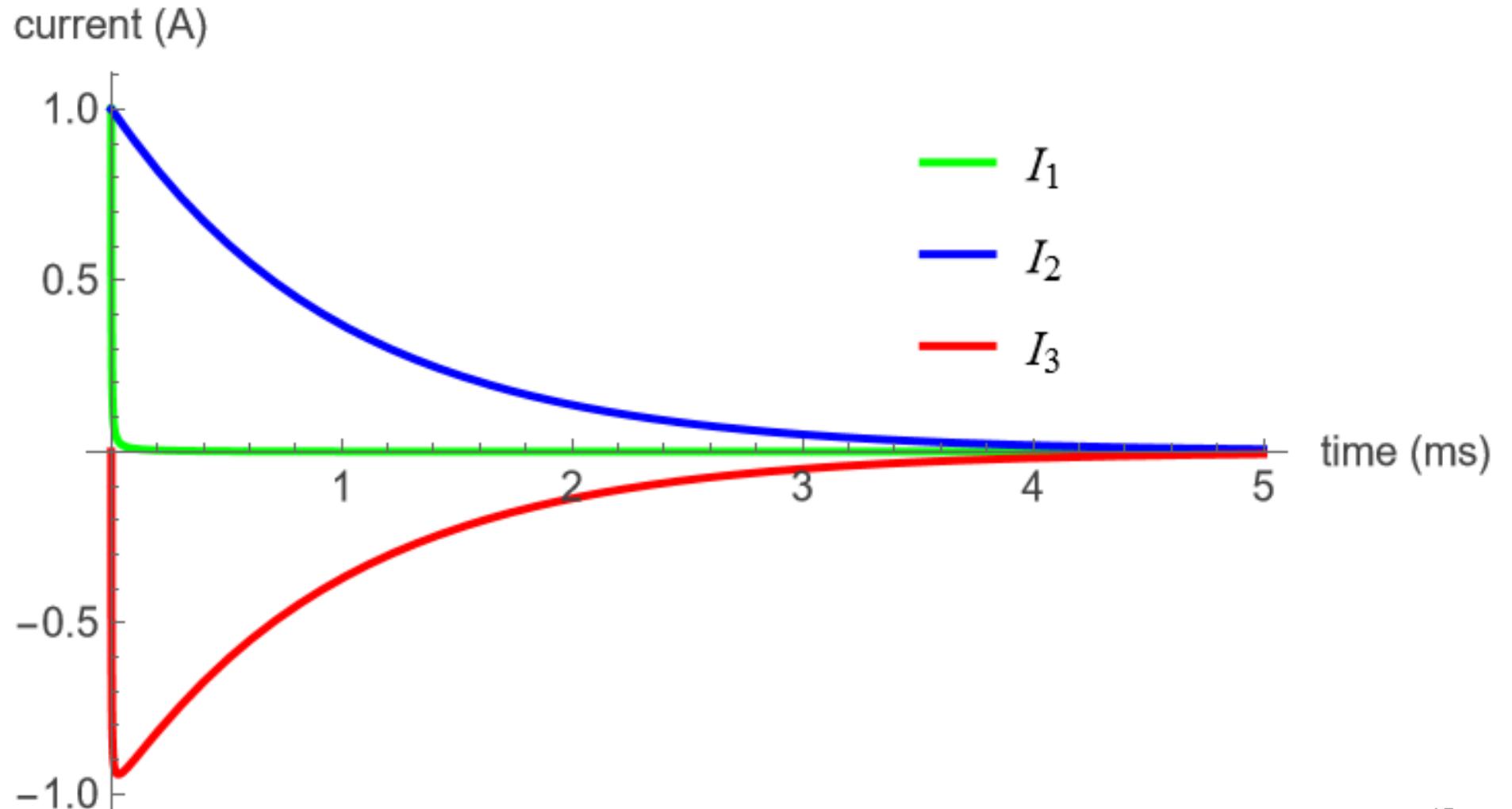


# CONCLUSIONS

## Circuit 1

Connecting two  $LR$  circuits in parallel with a battery and resistor gives coupled double-exponential currents. For the special case of identical coils we get symmetric and antisymmetric modes. We can decouple the two circuits by setting the battery resistance to zero.
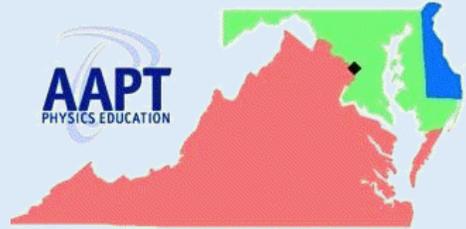
## Circuit 2

$LR$  circuits often require a “Make Before Break” switch to avoid problems. Another special one may be needed that could be called a “Smooth Transition” switch to avoid discontinuously jumping between zero and infinite resistance when it is opened or closed.



## Comments or questions?



[email: mungan@usna.edu](mailto:mungan@usna.edu)

[webpage: usna.edu/Users/physics/mungan](http://usna.edu/Users/physics/mungan)

where you can find the papers on which this presentation is based:

- *Physics Teacher* **43**, 519 (2005)
- *Physics Education* **59**, 023005 (2024)