



# Connecting an *RLC* Circuit to a Diode


*Carl Mungan*

*Volgenau Department of Physics, U.S. Naval Academy, Annapolis MD*

18 April 2026

Joint CSAAPT, AAPT-SEPS, NJAAPT Meeting at the University of Delaware

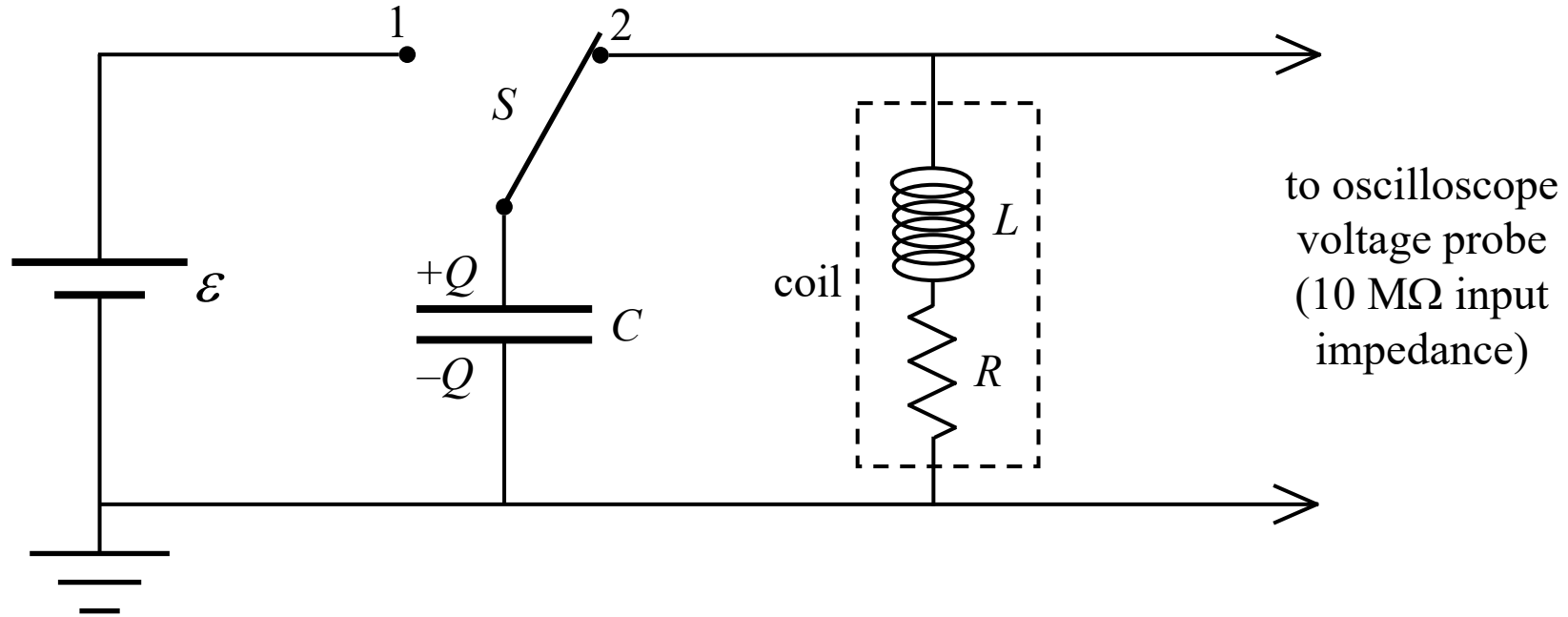The standard undriven series *RLC* circuit:



Switch  $S$  has been in position 1 for a long time so that  $Q_0 = C\varepsilon$ .  
Then at  $t = 0$  it is flipped to position 2.


experimental parameters:

$$L = 0.81\text{ H}$$

$$R = 62.7\ \Omega$$

$$C = 2.96\ \mu\text{F}$$


$$\varepsilon = 25.0\text{ V}$$

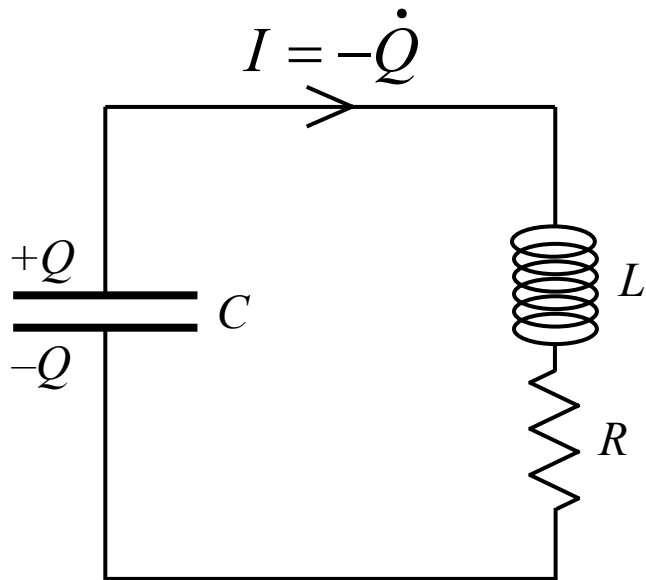

$$\frac{Q}{C} - L \frac{dI}{dt} - IR = 0$$

$$\div L \Rightarrow \boxed{\ddot{Q} + \frac{\dot{Q}}{\tau} + \omega^2 Q = 0}$$

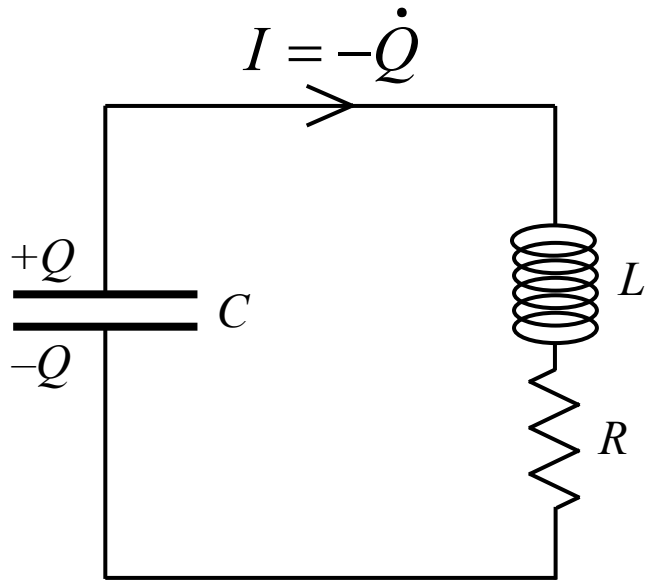where  $\omega \equiv \frac{1}{\sqrt{LC}}$  and  $\tau \equiv \frac{L}{R}$



$$\frac{Q}{C} - L \frac{dI}{dt} - IR = 0$$

$$\div L \Rightarrow \boxed{\ddot{Q} + \frac{\dot{Q}}{\tau} + \omega^2 Q = 0}$$

$$\text{where } \omega \equiv \frac{1}{\sqrt{LC}} \text{ and } \tau \equiv \frac{L}{R}$$

$$\text{solution: } \boxed{Q = A_0 e^{-t/2\tau} \cos(\omega' t - \phi)}$$

$$\text{where } \omega' \equiv \sqrt{\omega^2 - \frac{1}{(2\tau)^2}} \text{ which is underdamped if } \omega > \frac{1}{2\tau} \Rightarrow R \ll \sqrt{\frac{L}{C}} \approx 500 \Omega$$

Suggestion: Ask students to verify this soln by subbing it back into the above DE.

$$Q = A_0 e^{-t/2\tau} \cos(\omega' t - \phi)$$

fit  $A_0$  and  $\phi$  to IC:

$$Q(0) = Q_0 = C\varepsilon$$

$$I(0) = 0$$

The solution is NOT  $A_0 = Q_0$  and  $\phi = 0$ .

$$Q = A_0 e^{-t/2\tau} \cos(\omega' t - \phi)$$

fit  $A_0$  and  $\phi$  to IC:

$$Q(0) = Q_0 = C\varepsilon$$

$$I(0) = 0$$


The solution is NOT  $A_0 = Q_0$  and  $\phi = 0$ .

Instead it is

$$A_0 = Q_0 \frac{\omega}{\omega'}$$


$$\phi = \cos^{-1} \frac{\omega'}{\omega}$$

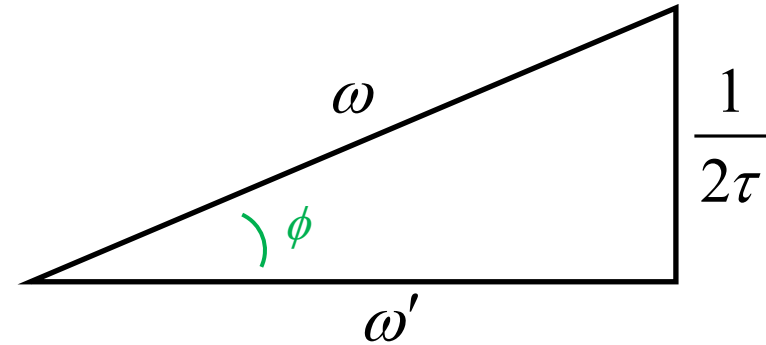as you may also wish  
to ask students to verify.




consistent with  $\omega' \equiv \sqrt{\omega^2 - \frac{1}{(2\tau)^2}}$

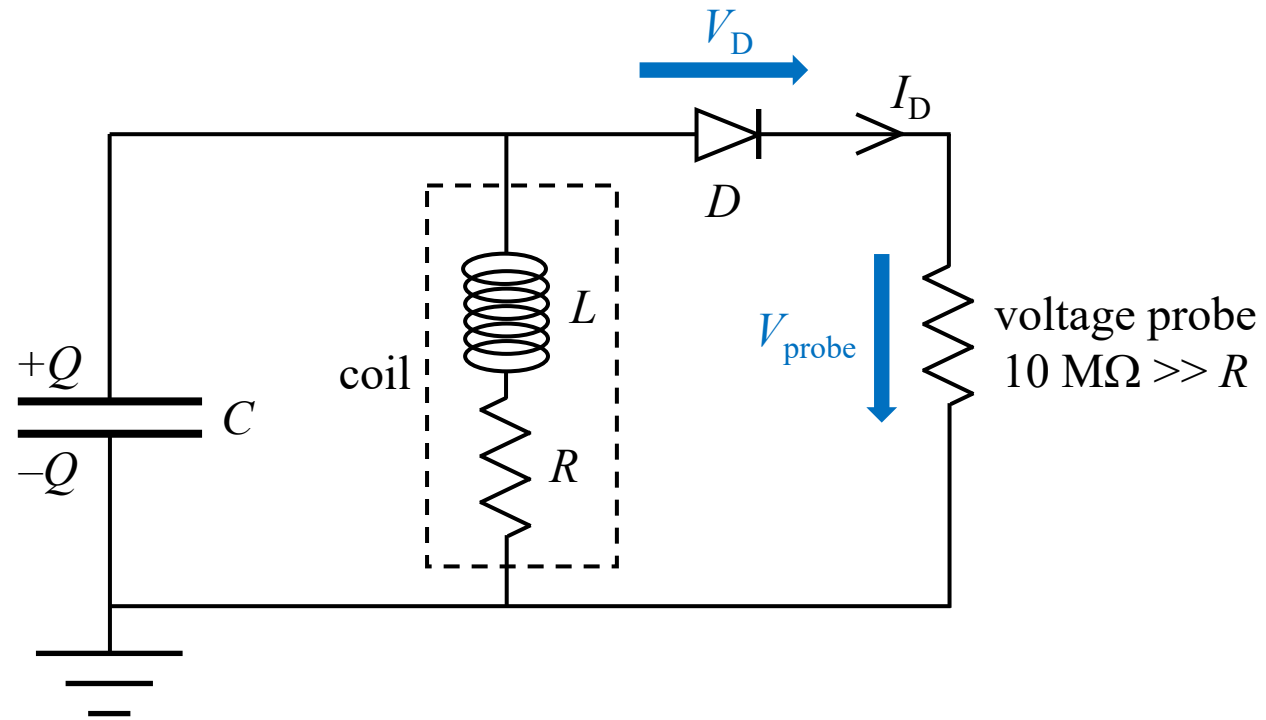
Next let's add a diode  $D$  into the circuit:



Start without the diode present. Then the voltage probe measures the underdamped  $RLC$  oscillations:
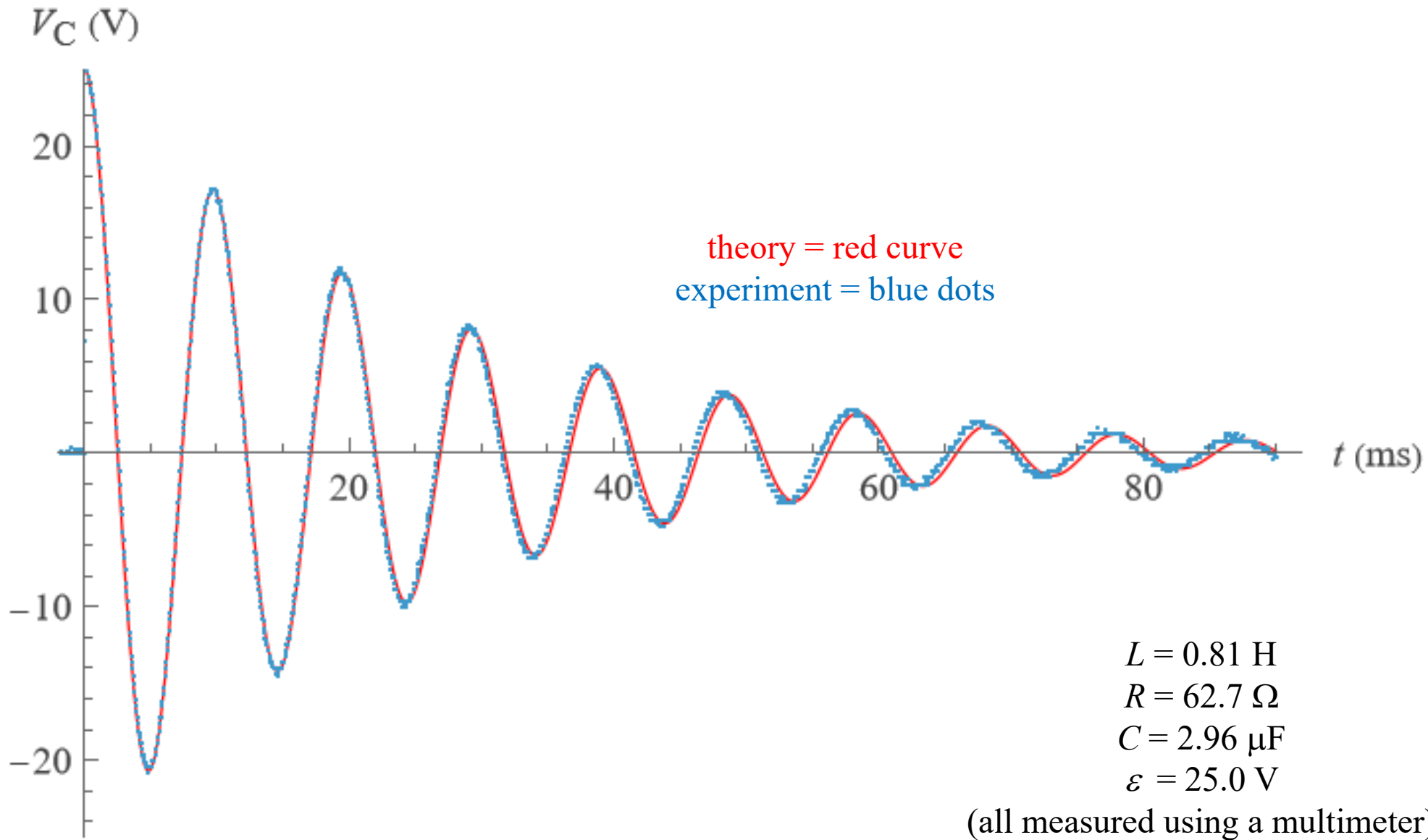
$$V_{\text{probe}} = V_C = Q / C \quad \text{where} \quad Q = Q_0 \frac{\omega}{\omega'} e^{-t/2\tau} \cos\left(\omega't - \cos^{-1} \frac{\omega'}{\omega}\right)$$



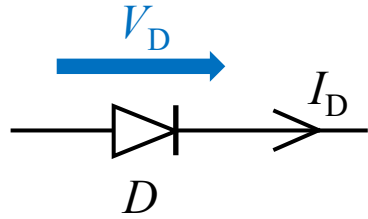


## Diode $I/V$ Characteristic

Perfect diode:


Ideal silicon diode:

Real silicon diode:

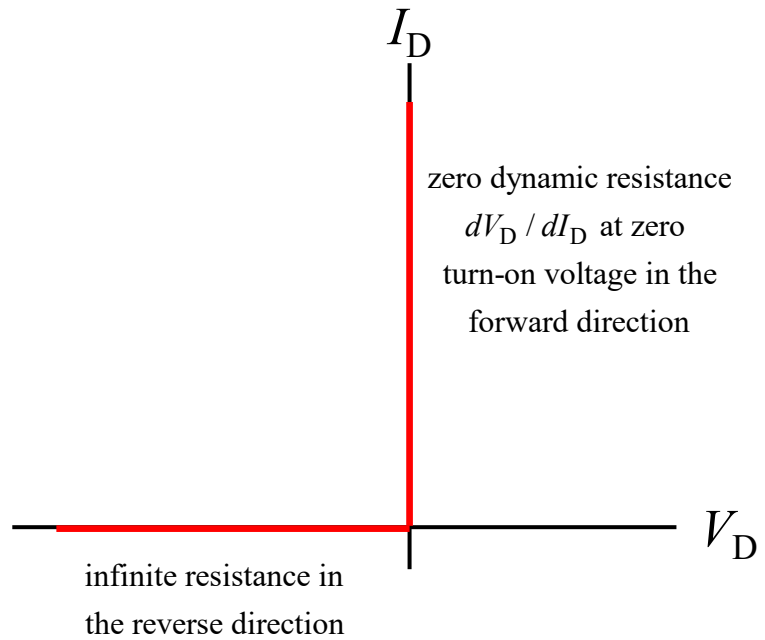

acts like a one-way valve


$V_{\text{probe}}$  (V)

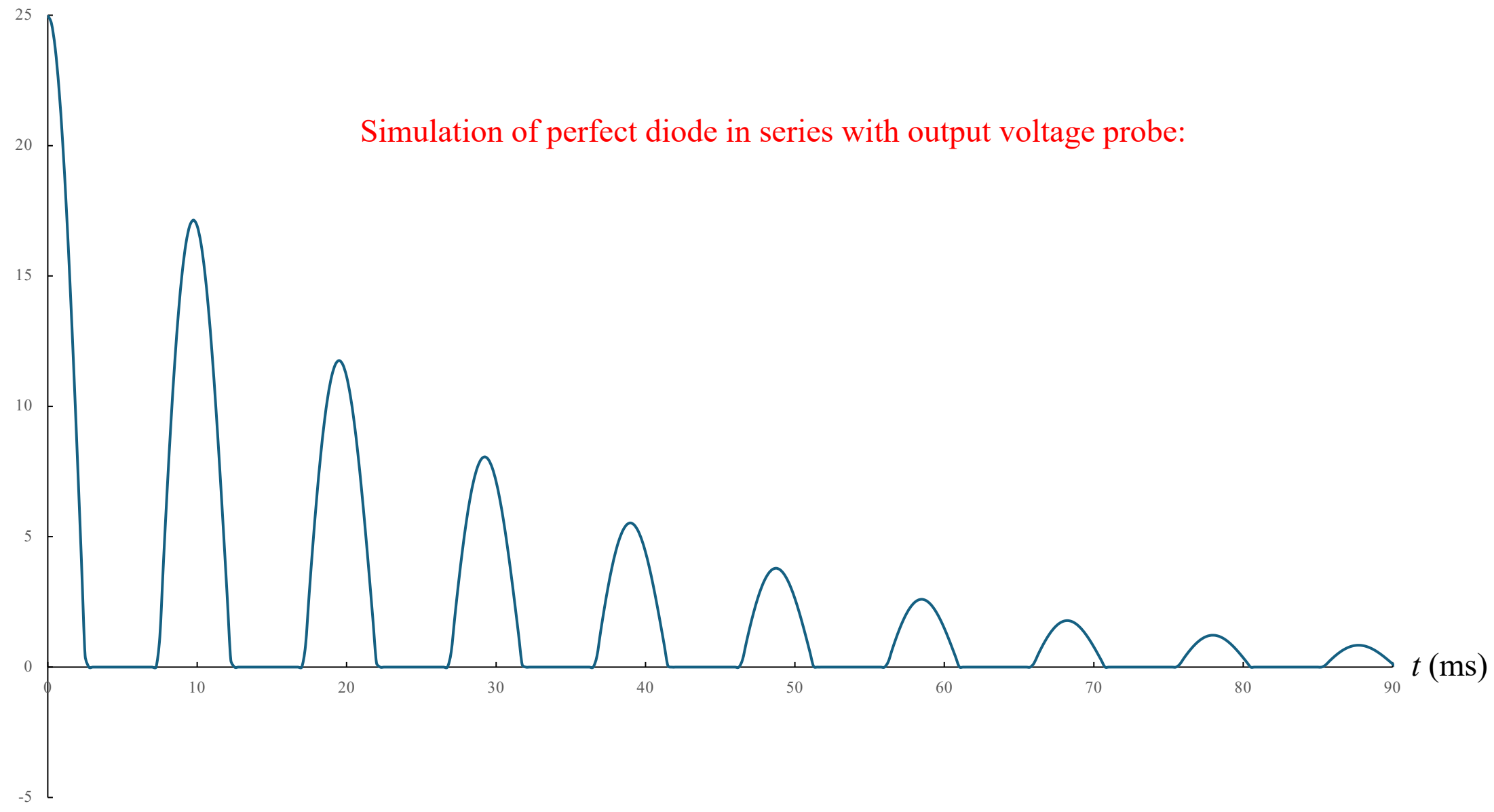

Simulation of perfect diode in series with output voltage probe:


That's not a very smooth rectified current.

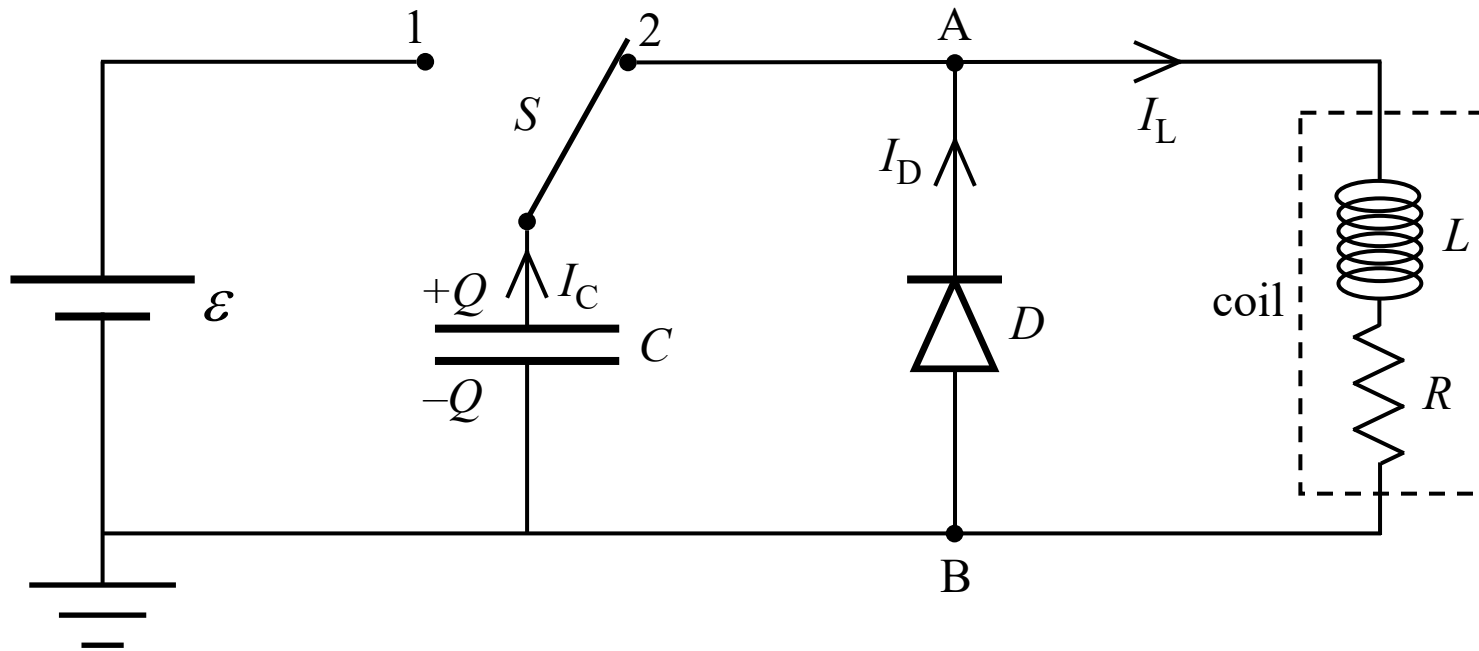What happens if instead of putting the diode in series with the output probe, we put it in parallel with it?




the voltage probe is connected between points A and B

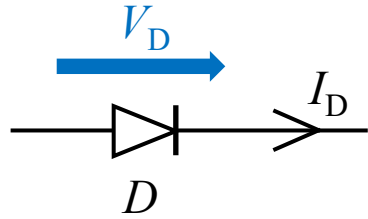Find DE for  $I_L$  using junction rule at A, loop rule for capacitor-diode loop, and loop rule for diode-coil loop.




## Diode $I/V$ Characteristic


Perfect diode:

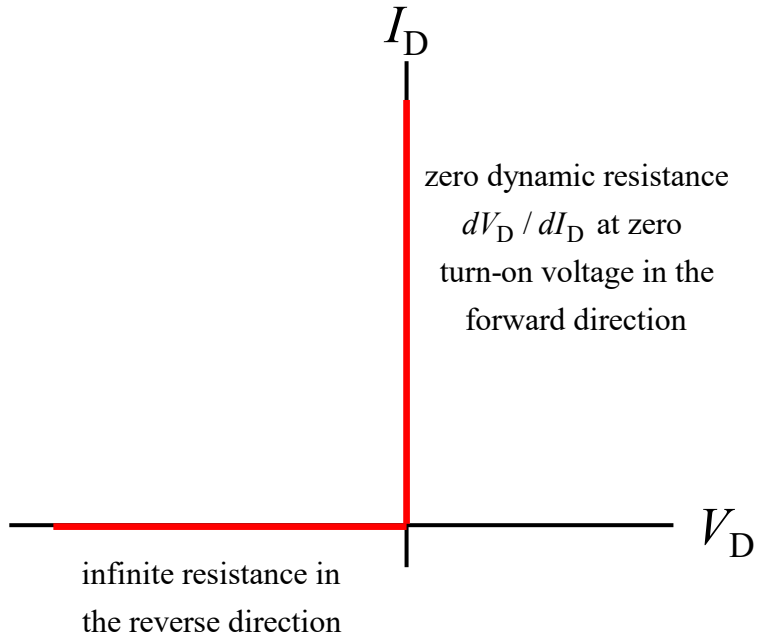

Ideal silicon diode:

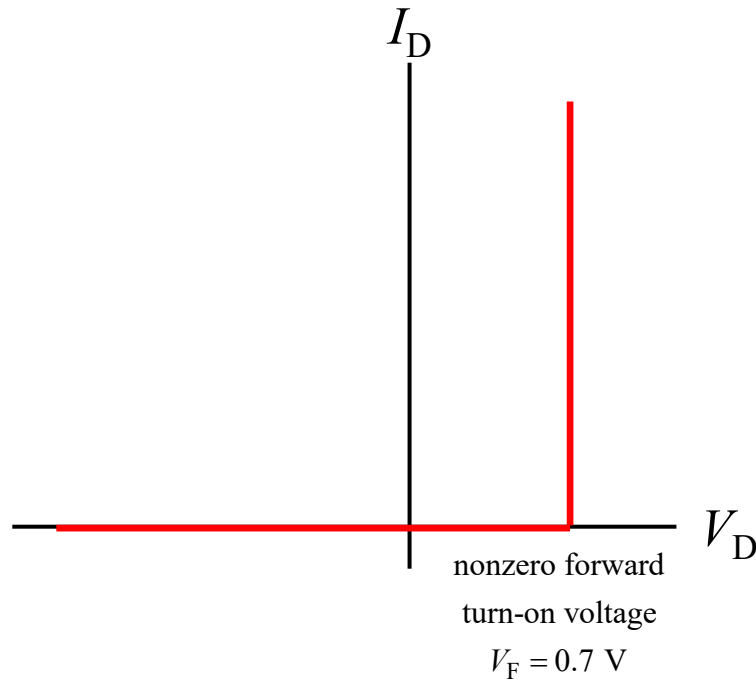


Real silicon diode:

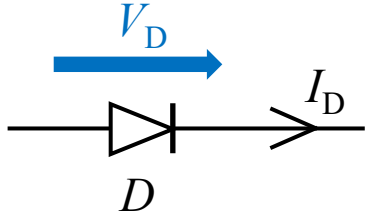


## Diode $I_V$ Characteristic


Perfect diode:

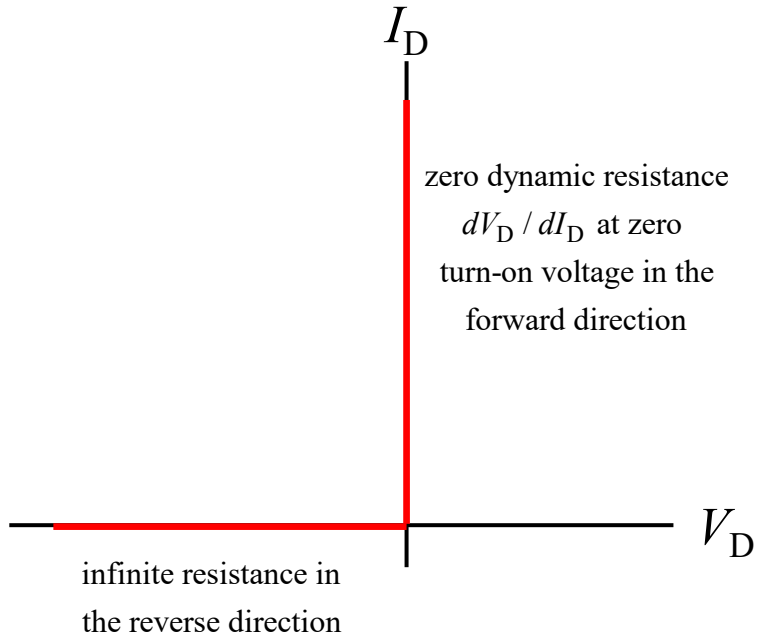

Ideal silicon diode:

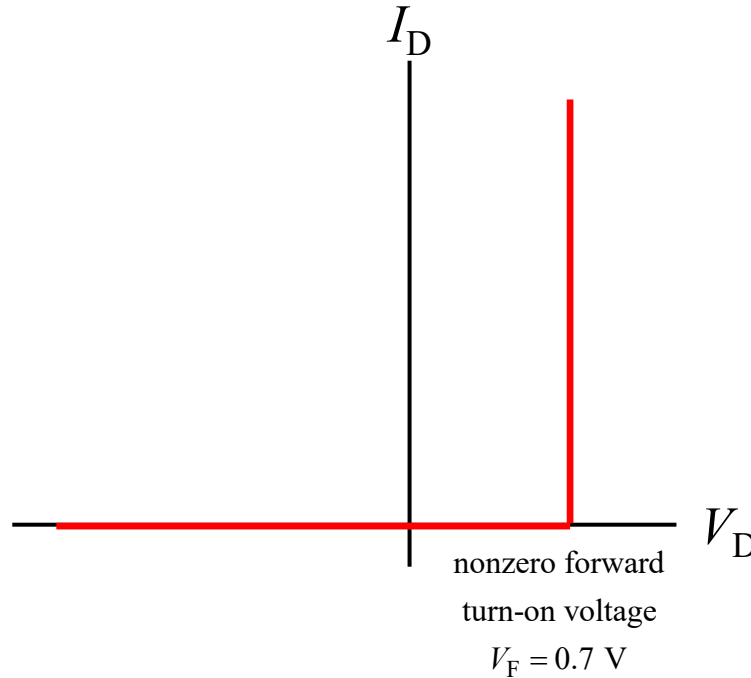

Real silicon diode:

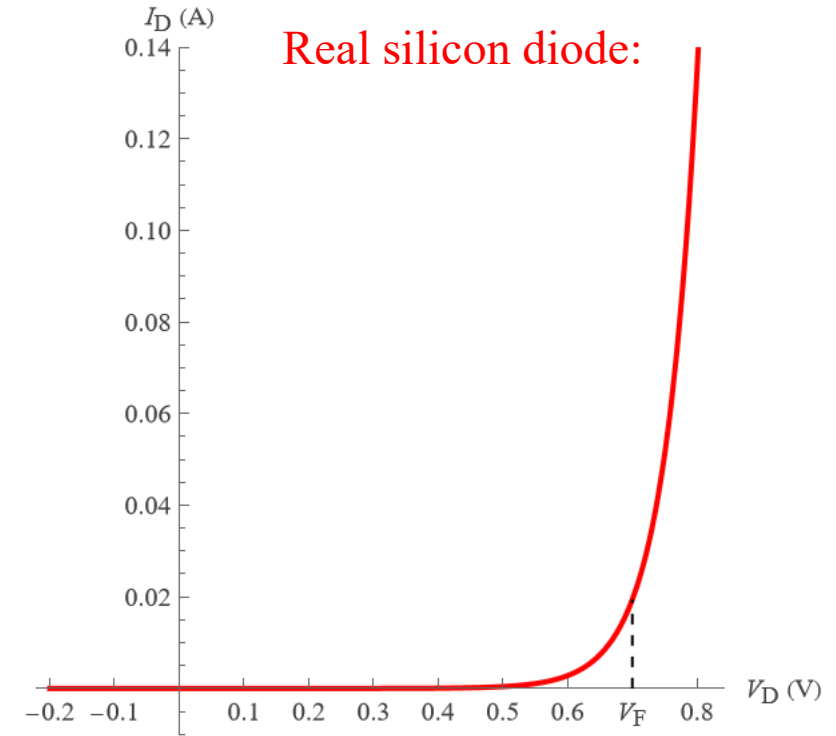

$$I_D = I_S [\exp(V_D / V_T) - 1]$$

where  $V_T = 2kT / e$  is the thermal voltage  
 and  $I_S = 25 \text{ nA}$  is the reverse saturation current  
 for a 1N4148 silicon diode

Resulting DE for the current through the coil:

$$LC\ddot{I}_L + RC\dot{I}_L + I_L = I_S \left[ \exp\left(-\frac{L\dot{I}_L + RI_L}{V_T}\right) - 1 \right]$$

(check: get the series  $RLC$  equation if  $I_S = 0$  in the absence of the diode)

which is solved numerically in Mathematica and then used to compute the voltage at the probe (or equivalently across the capacitor) as:

$$V_C = L\dot{I}_L + RI_L$$

Resulting DE for the current through the coil:

$$LC\ddot{I}_L + RC\dot{I}_L + I_L = I_S \left[ \exp\left(-\frac{L\dot{I}_L + RI_L}{V_T}\right) - 1 \right]$$


(check: get the series  $RLC$  equation if  $I_S = 0$  in the absence of the diode)

which is solved numerically in Mathematica and then used to compute the voltage at the probe (or equivalently across the capacitor) as:


$$V_C = L\dot{I}_L + RI_L$$

But before I show you the result for this voltage as a function of time, can you predict what it will look like?

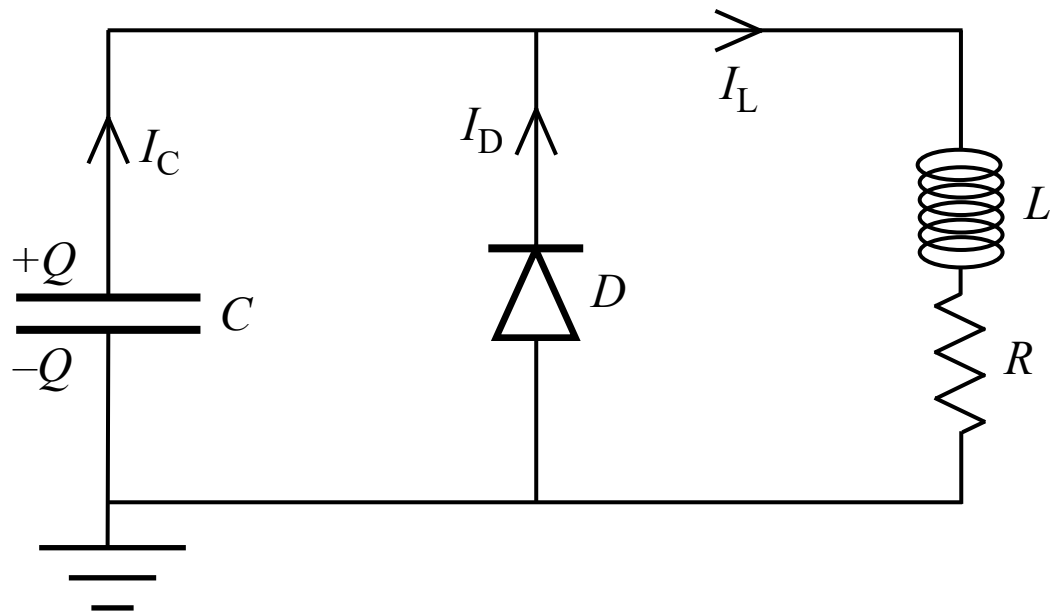(The oscilloscope is set to record a single trace when the switch is flipped from position 1 to 2.)



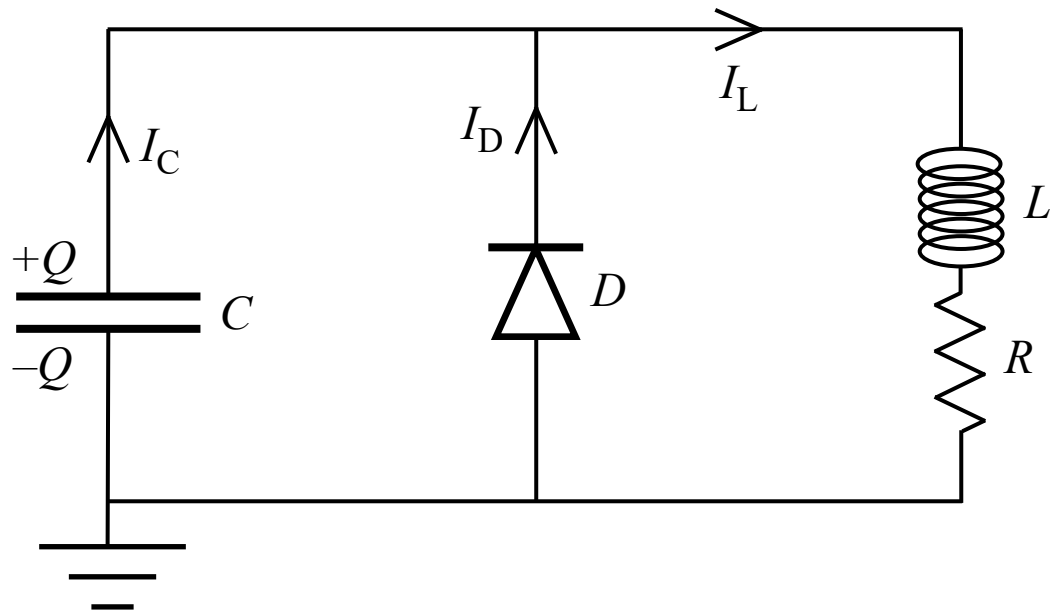
$$L = 0.81 \text{ H}$$
$$R = 62.7 \text{ } \Omega$$
$$C = 2.96 \text{ } \mu\text{F}$$
$$V_{C0} = 25.0 \text{ V}$$



$$\begin{aligned}L &= 0.81 \text{ H} \\R &= 62.7 \ \Omega \\C &= 2.96 \ \mu\text{F} \\V_{C0} &= 25.0 \text{ V}\end{aligned}$$

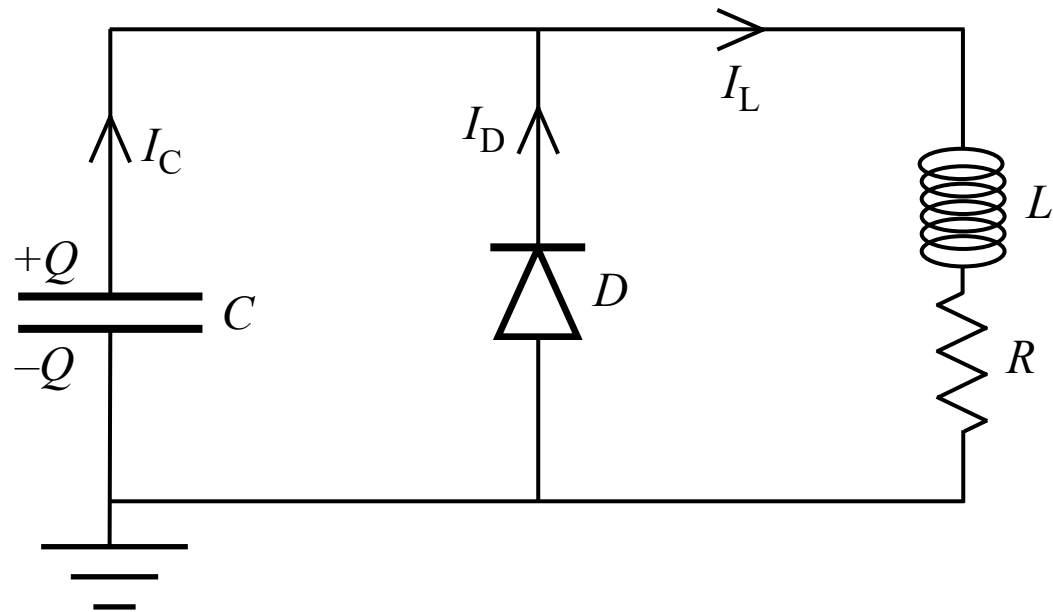The diode is initially reverse biased by 25 V so it is off.



$$L = 0.81 \text{ H}$$


$$R = 62.7 \text{ } \Omega$$

$$C = 2.96 \text{ } \mu\text{F}$$

$$V_{C0} = 25.0 \text{ V}$$

The diode is initially reverse biased by 25 V so it is off.

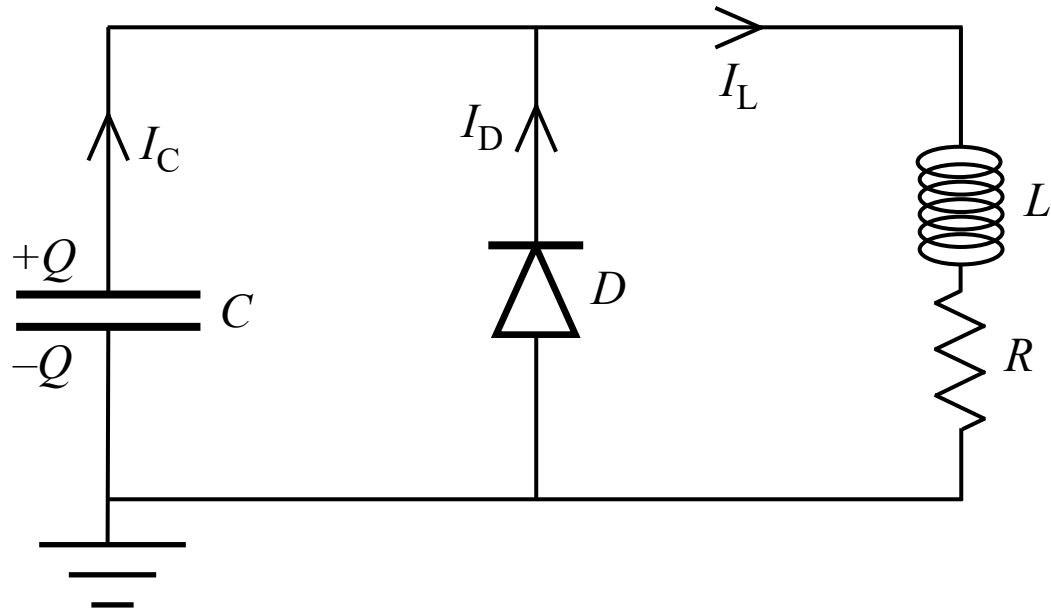Thus we get a bit more than a quarter cycle of an underdamped  $RLC$  oscillation through the capacitor and coil until  $V_C = -0.7 \text{ V}$  and  $I_L$  is just past maximum.



$$L = 0.81 \text{ H}$$

$$R = 62.7 \ \Omega$$

$$C = 2.96 \ \mu\text{F}$$


$$V_{C0} = 25.0 \text{ V}$$

The diode is initially reverse biased by 25 V so it is off.

Thus we get a bit more than a quarter cycle of an underdamped  $RLC$  oscillation through the capacitor and coil until  $V_C = -0.7 \text{ V}$  and  $I_L$  is just past maximum.

At that point the diode switches on and shorts out the capacitor. But the inductor keeps  $I_L$  going.

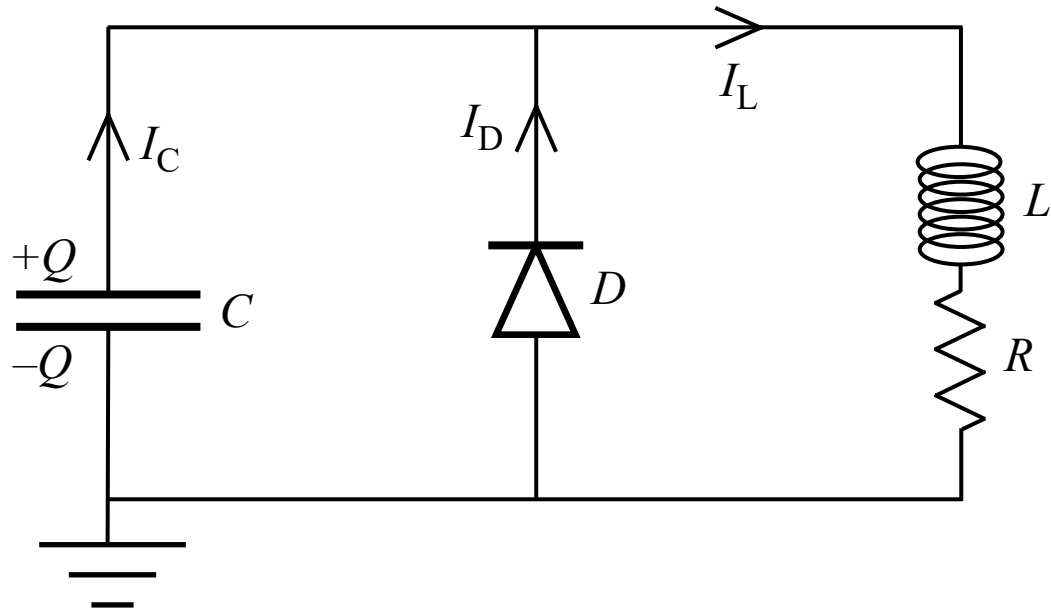**APPLICATION:** For a perfect diode and ideal inductor, we would have a long-lasting nearly constant current looping through the diode and coil.



$$L = 0.81 \text{ H}$$

$$R = 62.7 \ \Omega$$

$$C = 2.96 \ \mu\text{F}$$

$$V_{C0} = 25.0 \text{ V}$$


The diode is initially reverse biased by 25 V so it is off.


Thus we get a bit more than a quarter cycle of an underdamped  $RLC$  oscillation through the capacitor and coil until  $V_C = -0.7 \text{ V}$  and  $I_L$  is just past maximum.


At that point the diode switches on and shorts out the capacitor. But the inductor keeps  $I_L$  going.


**APPLICATION:** For a perfect diode and ideal inductor, we would have a long-lasting nearly constant current looping through the diode and coil.

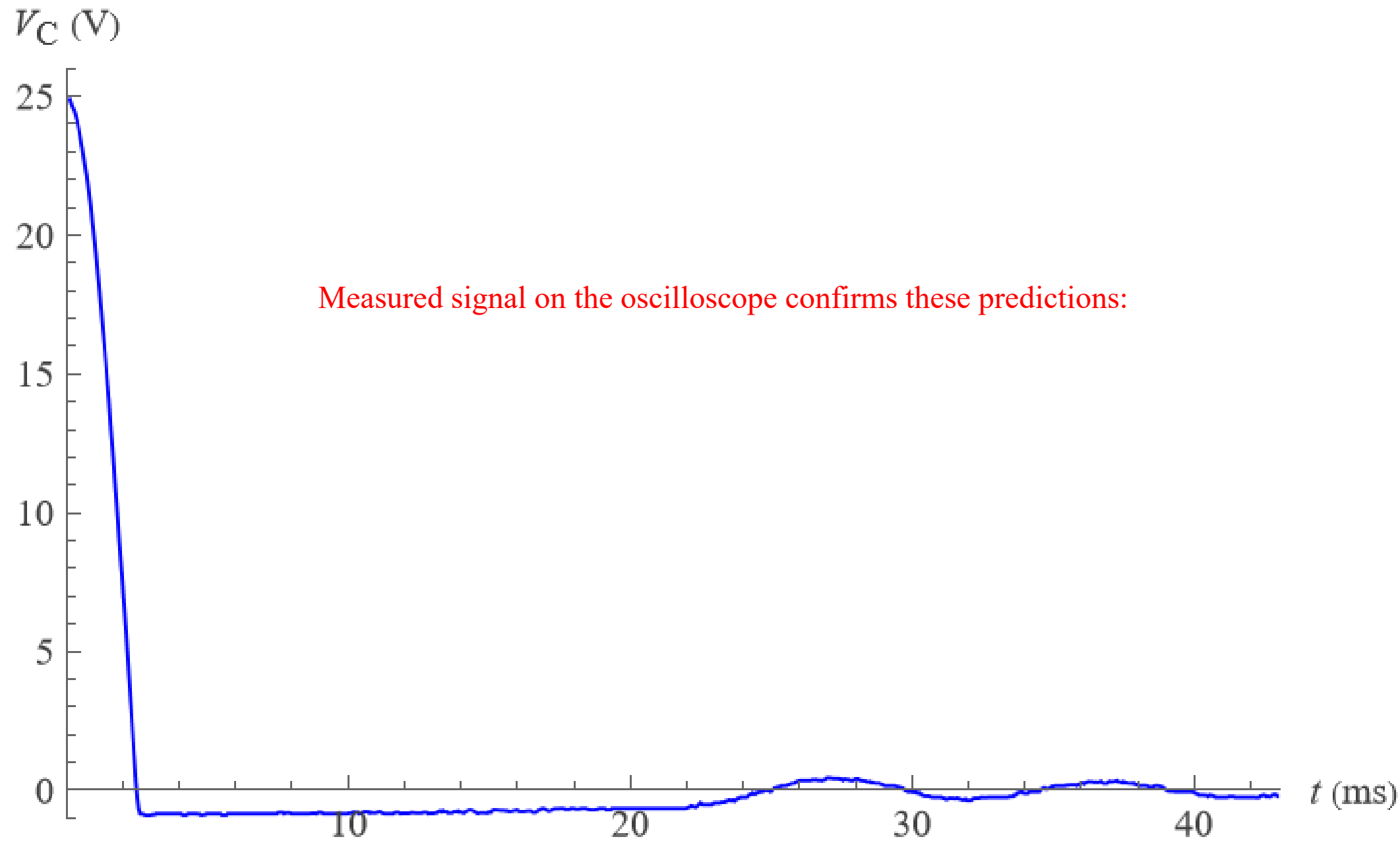However in the real world, the resistance of the coil and diode causes that current to slowly decay. The diode will then fall below its turn-on voltage and underdamped  $RLC$  oscillations will resume until the circuit is fully discharged.



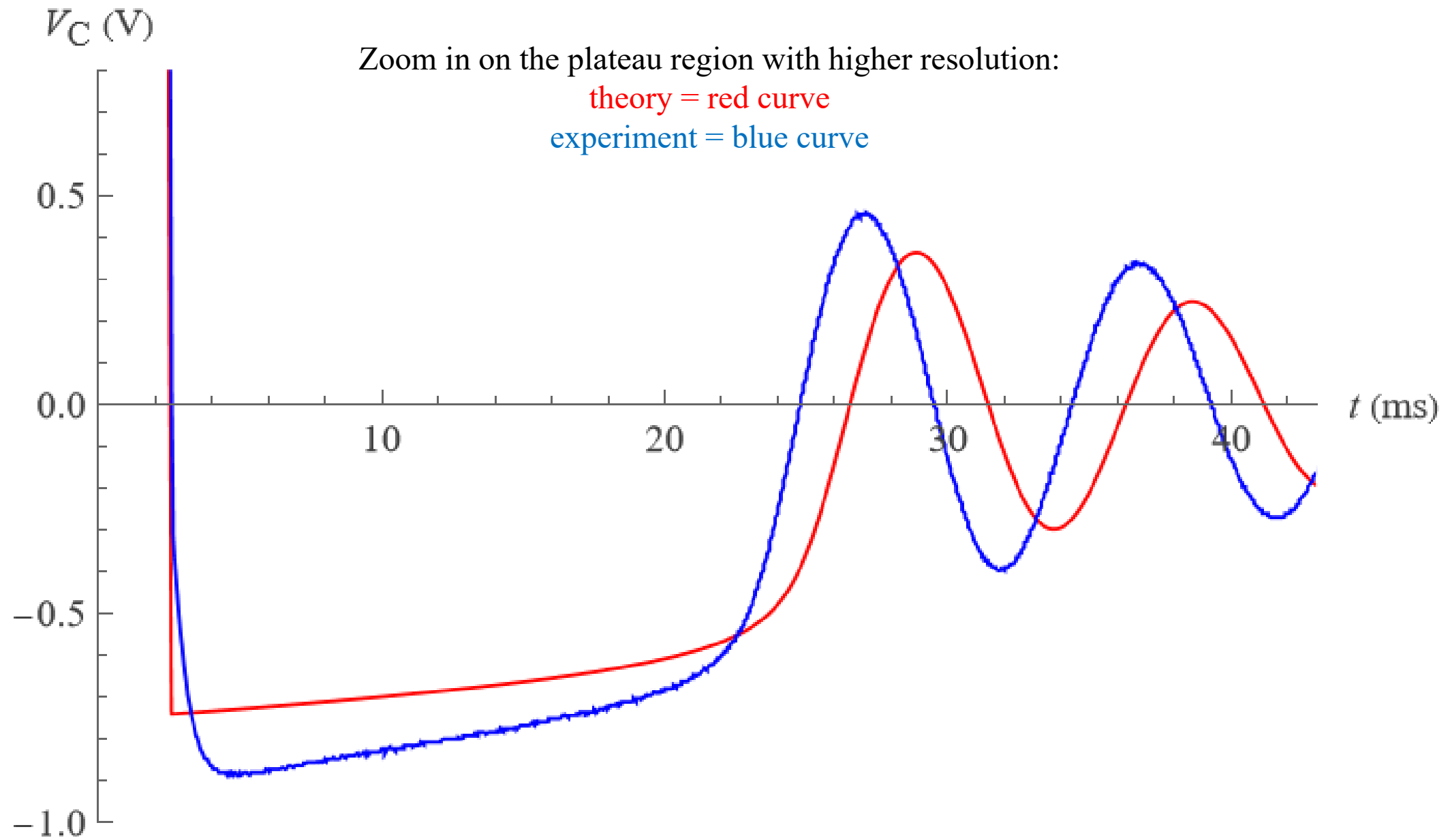

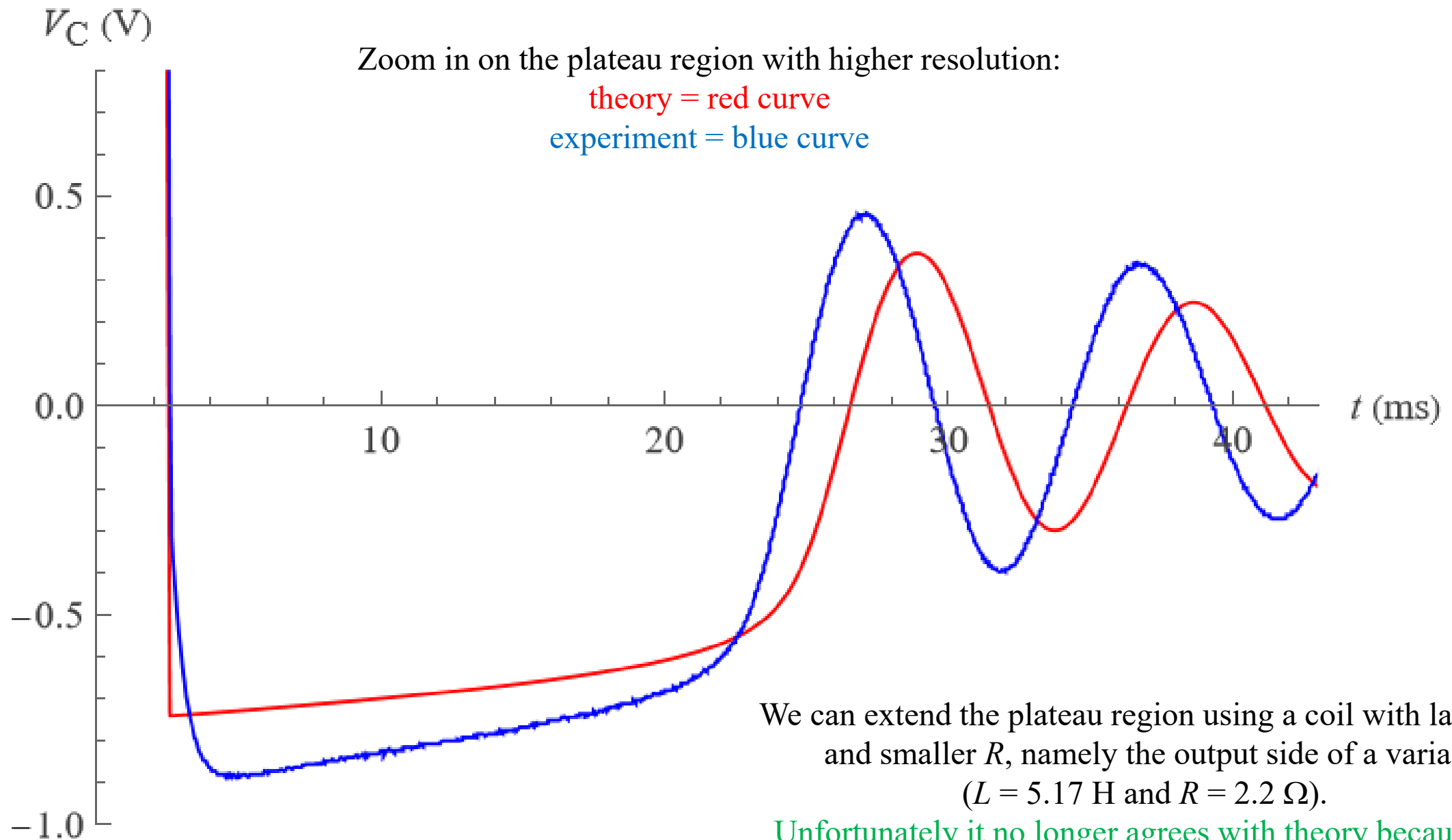

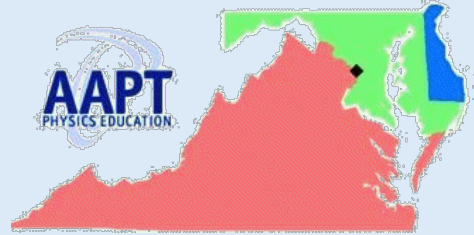

Comments or questions?



email: [mungan@usna.edu](mailto:mungan@usna.edu)


webpage: [usna.edu/Users/physics/mungan](http://usna.edu/Users/physics/mungan)

where you can find the article on which this presentation is based:


“Flattening the oscillations of an underdamped RLC circuit using a diode,”  
European Journal of Physics 47, 025207 (2026)

Extra slides

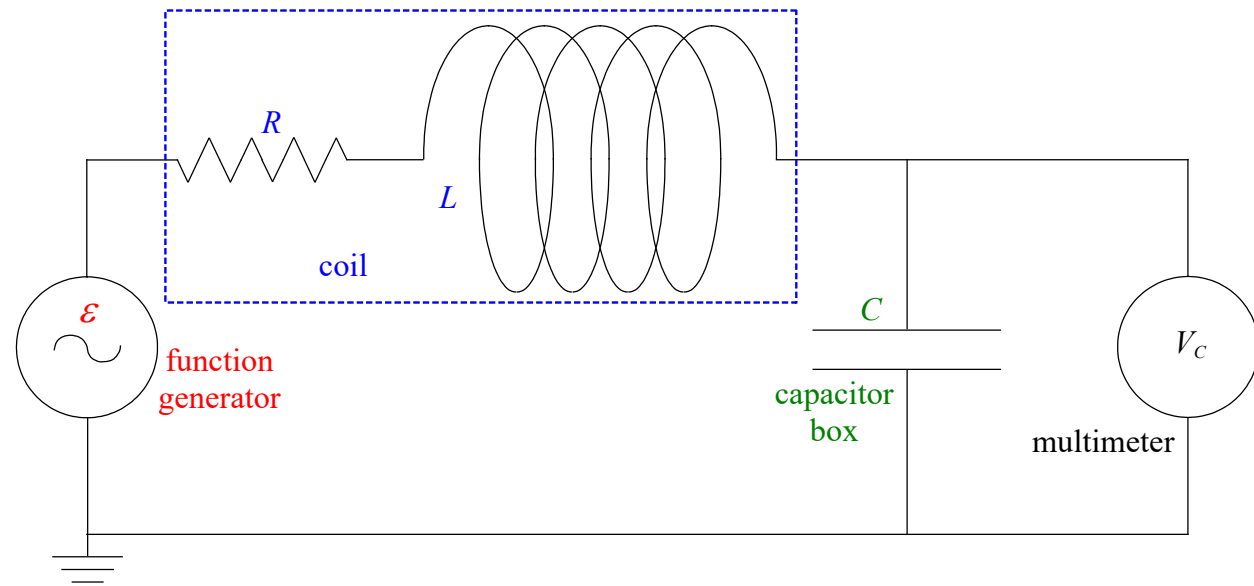experiment: *Simple but accurate driven RLC experiment*, Phys. Educ. **57**, 053002 (2022)




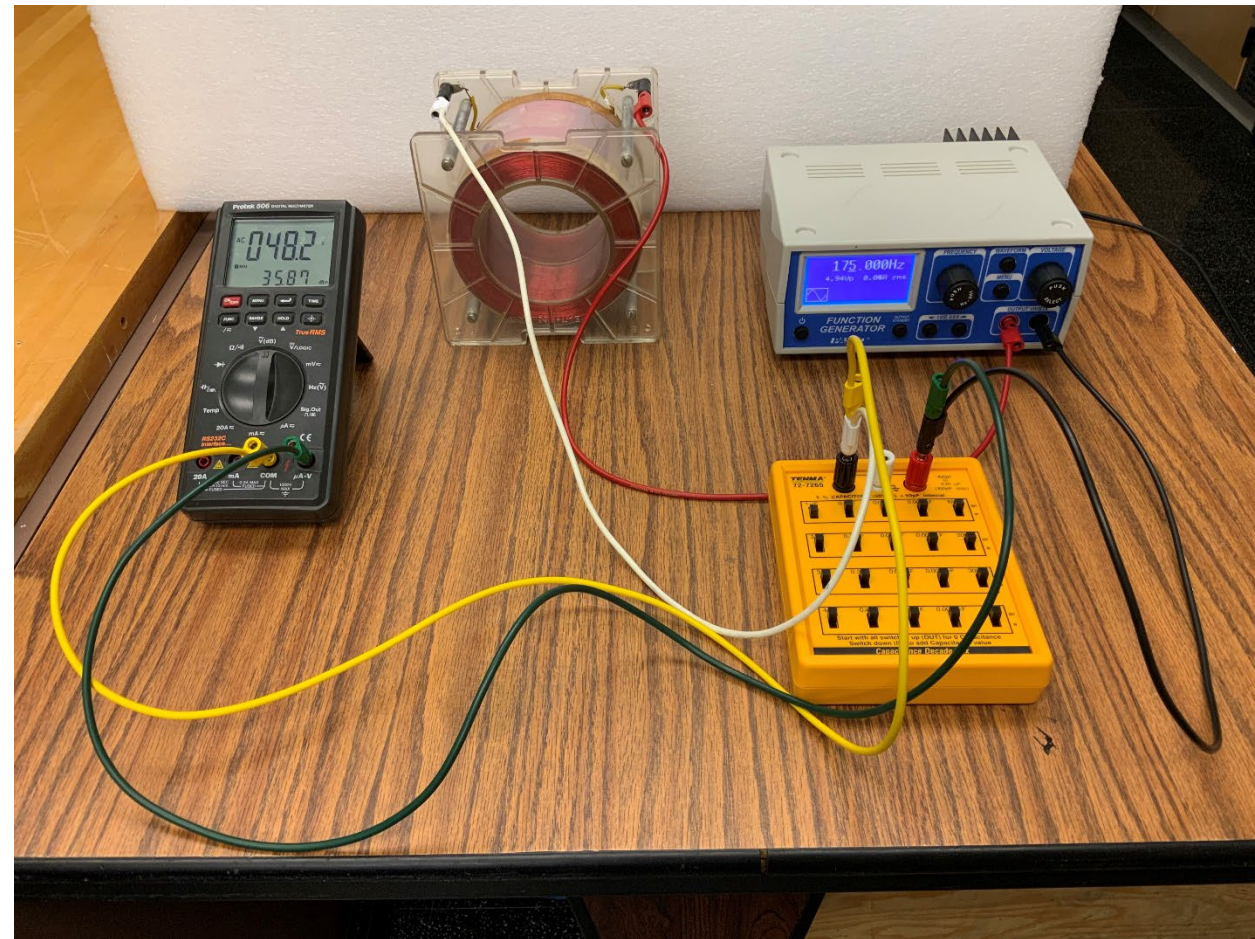fix the function generator output voltage at 3.5 V





Consider a parallel *RLC* circuit:

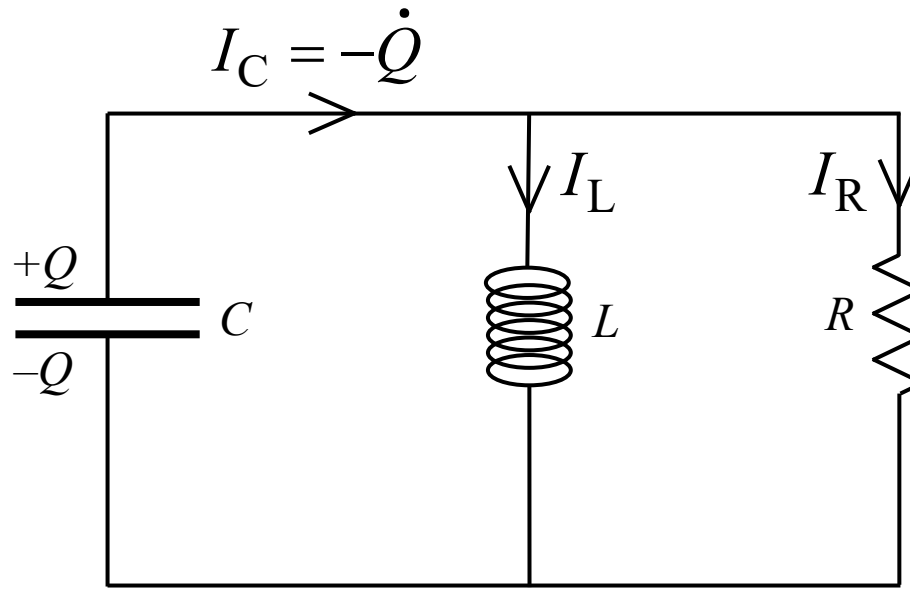

junction rule  $I_C = I_L + I_R \Rightarrow \dot{Q} + I_L + I_R = 0$  (by subbing in  $I_C$ )

outer loop  $\frac{Q}{C} = RI_R \Rightarrow \ddot{Q} + \dot{I}_L + \frac{\dot{Q}}{\tau} = 0$  ( $\div R$ , sub in  $I_R$ ,  $\tau \equiv RC$ , time deriv)

left loop  $\frac{Q}{C} = L \frac{dI_L}{dt} \Rightarrow \boxed{\ddot{Q} + \frac{\dot{Q}}{\tau} + \omega^2 Q = 0}$  ( $\div L$ , sub in  $\dot{I}_L$ ,  $\omega \equiv \frac{1}{\sqrt{LC}}$ )

We get the SAME equation as for a series *RLC* circuit!

The only differences are now  $\tau = RC$  instead of  $\tau = L / R$  and the oscillations are underdamped (i.e., real  $\omega'$ ) when

$$\omega > \frac{1}{2\tau} \quad \Rightarrow \quad R \gg \sqrt{\frac{L}{C}} \approx 500 \, \Omega \quad \text{instead of} \quad R \ll \sqrt{\frac{L}{C}}.$$

It makes sense that  $R$  needs to be small for the series circuit and large for the parallel circuit, so that the resistor only makes a small disturbance to the  $LC$  oscillations.